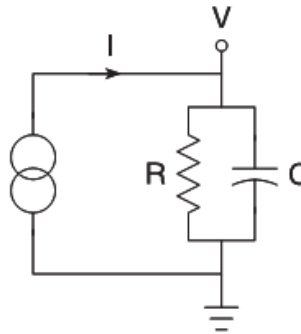


Lab 2 – Passive membrane properties

****make sure to include all generated figures and discuss results****

1. Passive membrane properties as RC circuit.


Open the Matlab m-file “rc.m”. In this simulation, we will investigate how the membrane potential responds to a steady current input. Here, the membrane potential is modeled using the parallel RC equivalent circuit model.



- 1a. Run the model with the default parameters ($R = 10 \text{ M}\Omega$, $C = 1 \text{ }\mu\text{F}$, $I = 1 \text{ nA}$) and describe the output. What is the steady state voltage? Approximately how long does it take the membrane potential to reach steady state (>99% of the steady state voltage)?
 *Note: For all questions, adjust the x and y axes on your plots appropriately before pasting them into your lab notebook.
- 1b. Resetting to the default values each time ($R = 10 \text{ M}\Omega$, $C = 1 \text{ }\mu\text{F}$, $I = 1 \text{ nA}$), determine what effects the following parameters have on the resulting membrane potential time course and steady state values (make sure to describe the effects):
 - i. Multiplying R by 5
 - ii. Dividing C by 10
 - iii. Multiplying R by 10 and dividing C by 10
- 1c. A way in which the time constant τ can be obtained when either R or C or both are uncertain is to measure the time after constant current onset where the membrane potential reaches approximately 63.2% of its steady state value (Hint: $0.632 \cdot V_{ss} = 0.632 \cdot I_{stim} \cdot R$). Test this by varying the input current, the resistance and the capacitance and compare the measured values of τ (remember the stimulus is turned on at $t = 10 \text{ sec}$!) to the theoretical values obtained from $\tau = R \cdot C$. Provide a table with the column headers below to display your input parameters and results for at least 6 trials. Provide a theoretical justification for why this method works.

Istim	R	C	τ	Vss	$0.632 \cdot V_{ss}$	Time at $0.632 \cdot V_{ss}$
-------	---	---	--------	-----	----------------------	------------------------------

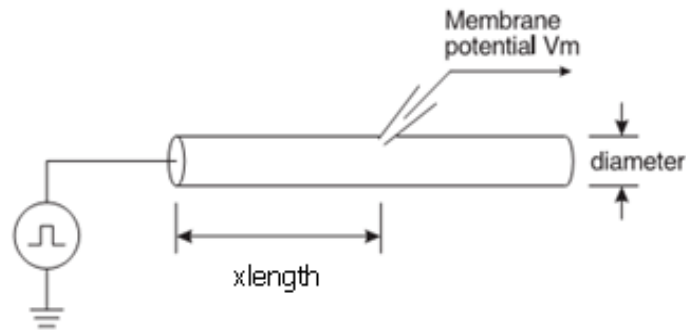2. Investigating the Effects of Axial Resistance



Open the Matlab m-file “axialResistance.m”. In this simulation, we will investigate how the membrane potential changes along the length of a semi-infinite cable, when we inject current at location $x = 0$.

- 2a. Run the model with the default parameters and describe how the membrane potential responds to a current step input delivered at $t = 10$ sec.
- 2b. Plot the steady state voltage for each location in 2a. What is the theoretical relationship (equation) between x and the steady state voltage? Add the theoretical relationship to your plot.
- 2c. Change the locations at which the voltage is being recorded by changing the “ x ” parameter (NOTE: keep the leading 0 in the $x = [0 \dots]$ expression). At what distance from the current input is the steady state voltage reduced to $1/e$ of its original value (e.g. the length constant ‘ λ ’)? How does this compare to the theoretical value of the length constant?
- 2d. What is the steady state membrane potential at a distance of one-fifth the length constant?
- 2e. Explain why there is a difference in steady state membrane potential between a location close to and a location far away from the current injection site.
- 2f. Using the results from the above steps, if this neuron used passive signaling instead of action potentials to communicate with a downstream neuron 5 mm away, what would the steady state membrane potential be at the terminal between the two neurons? Is this an effective communication strategy?
- 2g. There are a wide variety in geometries of axonal and dendritic processes amongst the various neuron morphologies, ranging from very small ($< 1 \mu\text{m}$) to very large (1 mm) diameters. With your voltage probe fixed at a distance of 1 mm from the current injection site, determine the effects of increasing the radius (variable “ a ”). Test many values of a , ranging from a very small radii to radii values much greater than what are naturally observed. Plot each peak (steady state) voltage measured as a function of the length constant, λ . Describe the relationship between the steady state voltage and the length constant.