

# Lecture 2

## Equivalent Circuits

# What is missing from our models?

- We can use Nernst and Goldman to predict a neuron's membrane potential when the net flux (net current) is zero.
- What happens in the dynamic state, when the net current is not zero? For example, if we inject current into our isopotential neuron model?

We will apply basic principles of RC circuits to predict  $V_m$  across time.

First, let's quickly review RC circuits.

# Resistance

For a cylindrical block

$$R = \rho l / A$$




- $\rho$  is resistivity ( $\Omega\text{cm}$ )
- $l$  is length of the cable (cm)
- $A$  is cross sectional area ( $\text{cm}^2$ )

# Resistance

For a cylindrical block

$$R = \rho l / A$$

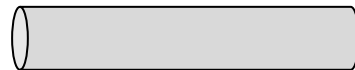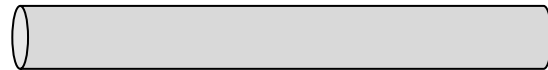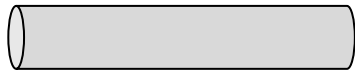- $\rho$  is resistivity ( $\Omega\text{cm}$ )
- $l$  is length of the cable (cm)
- $A$  is cross sectional area ( $\text{cm}^2$ )




# Resistance


For a cylindrical block

$$R = \rho l / A$$

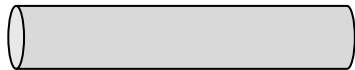- $\rho$  is resistivity ( $\Omega\text{cm}$ )
- $l$  is length of the cable (cm)
- $A$  is cross sectional area ( $\text{cm}^2$ )



$$R_1 < R_2$$

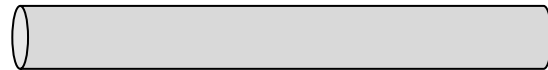


# Resistance



For a cylindrical block

$$R = \rho l / A$$

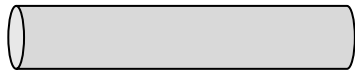- $\rho$  is resistivity ( $\Omega\text{cm}$ )
- $l$  is length of the cable (cm)
- $A$  is cross sectional area ( $\text{cm}^2$ )



$$R_1 < R_2$$

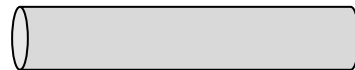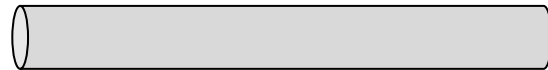

$$R_1 > R_2$$



# Resistance

For a cylindrical block

$$R = \rho l / A$$

- **$\rho$  is resistivity ( $\Omega\text{cm}$ )**
- $l$  is length (cm)
- $A$  is cross sectional area ( $\text{cm}^2$ )

The resistivity of mammalian saline is  $60 \Omega\text{cm}$ , while the resistivity of a pure phospholipid bilayer can reach  $10^{15} \Omega\text{cm}$ .



# Ohm's Law



$$V=IR$$

or


$$V=I/G$$

- $R$  is resistance (in ohms,  $\Omega$ )
- $G$  is conductance (in siemens, S)
- $V$  is potential difference (in volts, V)
- $I$  is current (in amperes, A)
- Remember  $R=1/G$



# Injecting current across a resistor

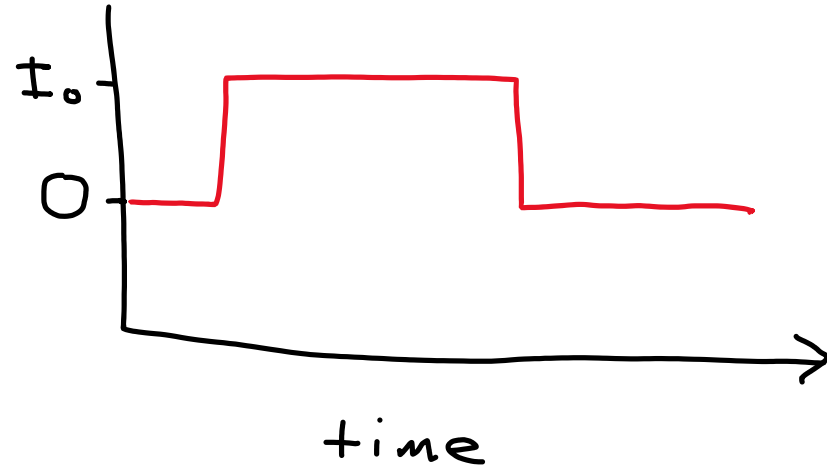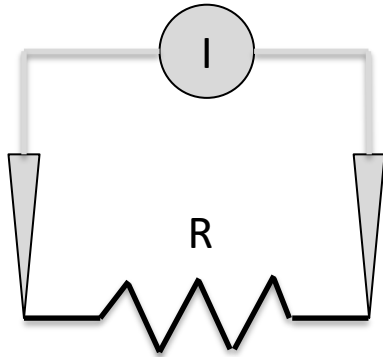


# Injecting current across a resistor

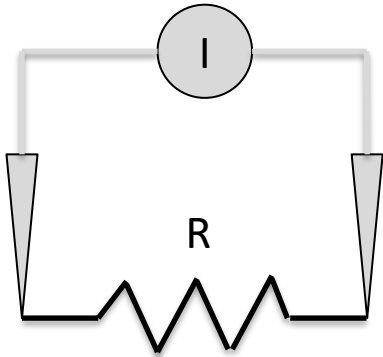

$V=?$

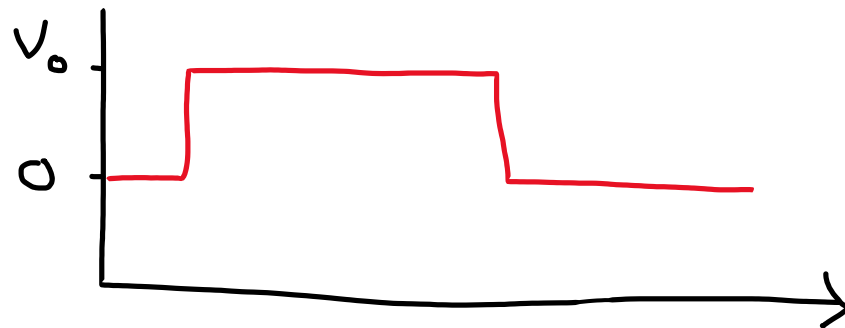
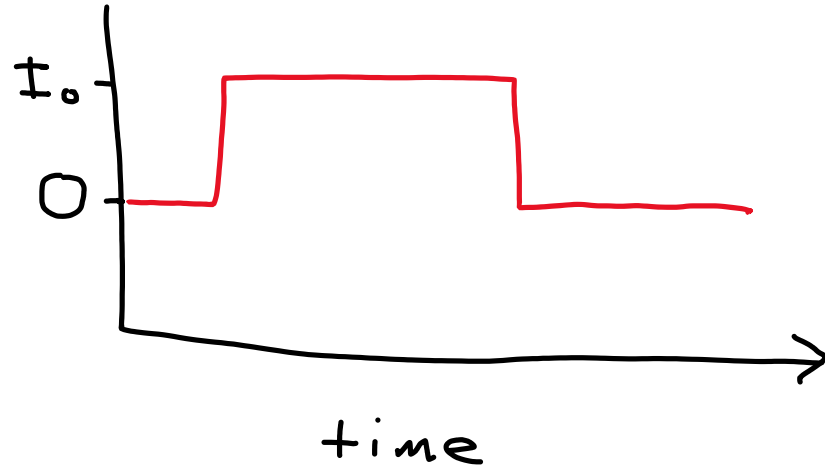


# Injecting current across a resistor

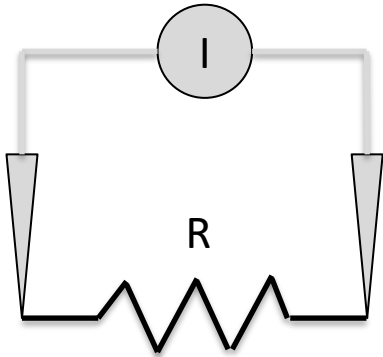


$V=?$

$$V_0 = I_0 R$$

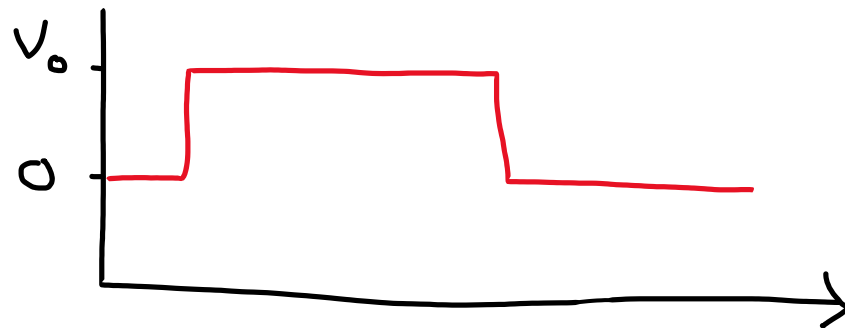
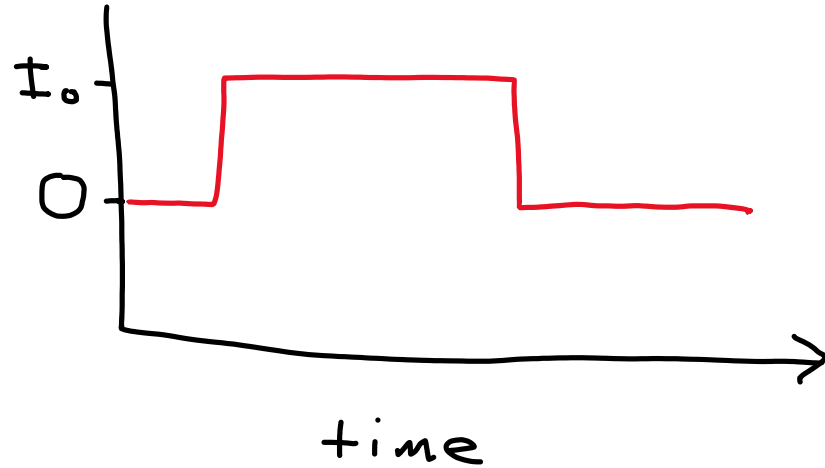


# Clamping the voltage across a resistor

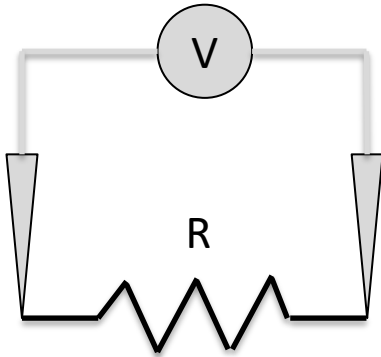

$I = ?$

$$I_0 = V_0 / R$$

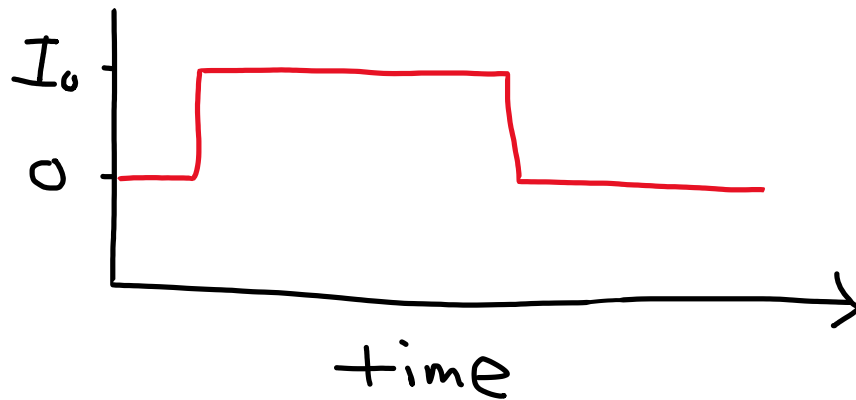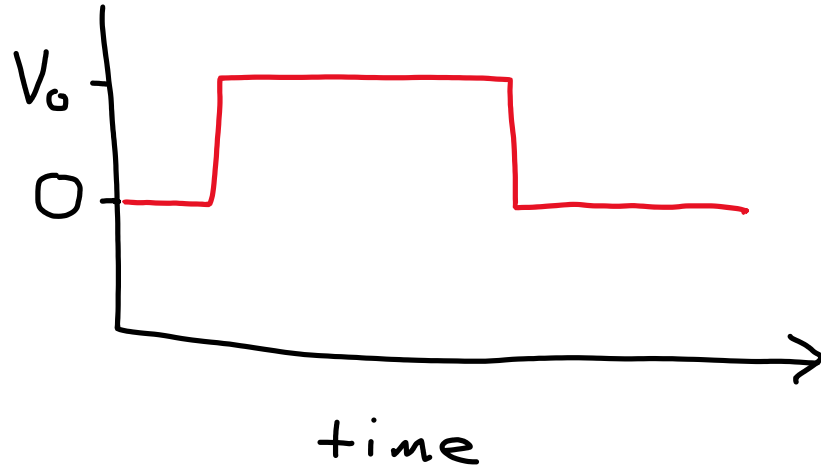

# Capacitance

Simple capacitor:

- Two parallel plate conductors of area  $A$
- Conductors are separated by an insulator of thickness  $d$  and dielectric constant  $\epsilon$  ( $\text{CV}^{-1}\text{m}^{-1}$ )
- Where  $\epsilon_0$  is the natural constant


$$C = \frac{\epsilon\epsilon_0 A}{d}$$

# Capacitance

Simple capacitor:

- Two parallel plate conductors of area  $A$
- Conductors are separated by an insulator of thickness  $d$  and dielectric constant  $\epsilon$  ( $\text{CV}^{-1}\text{m}^{-1}$ )
- Where  $\epsilon_0$  is the natural constant

$$C = \frac{\epsilon\epsilon_0 A}{d}$$

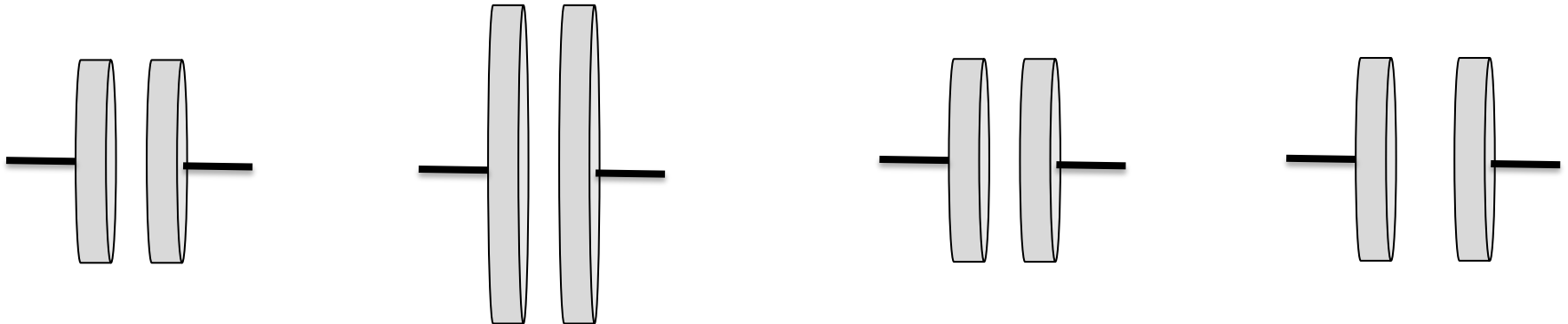


# Capacitance

Simple capacitor:

- Two parallel plate conductors of area  $A$
- Conductors are separated by an insulator of thickness  $d$  and dielectric constant  $\epsilon$  ( $\text{CV}^{-1}\text{m}^{-1}$ )
- Where  $\epsilon_0$  is the natural constant

$$C = \frac{\epsilon\epsilon_0 A}{d}$$

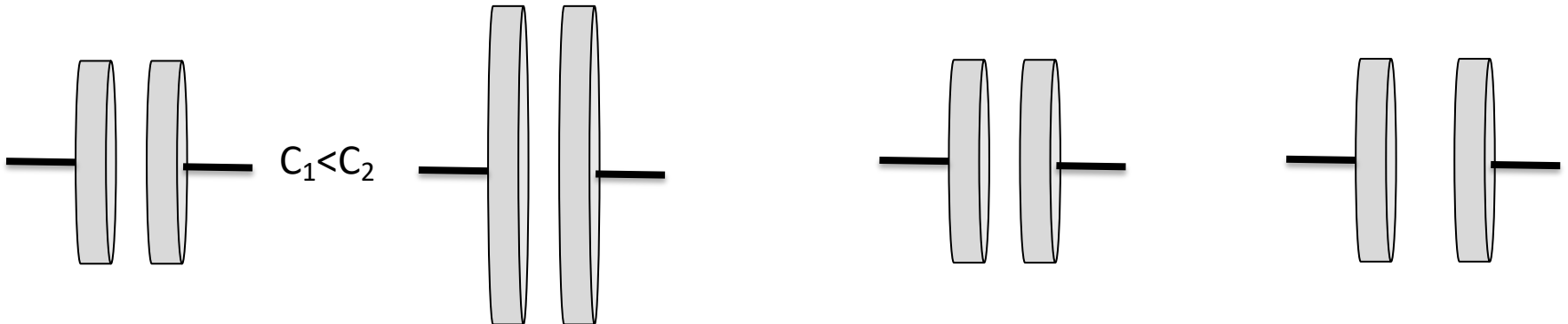




# Capacitance

Simple capacitor:

- Two parallel plate conductors of area  $A$
- Conductors are separated by an insulator of thickness  $d$  and dielectric constant  $\epsilon$  ( $\text{CV}^{-1}\text{m}^{-1}$ )
- Where  $\epsilon_0$  is the natural constant

$$C = \frac{\epsilon\epsilon_0 A}{d}$$

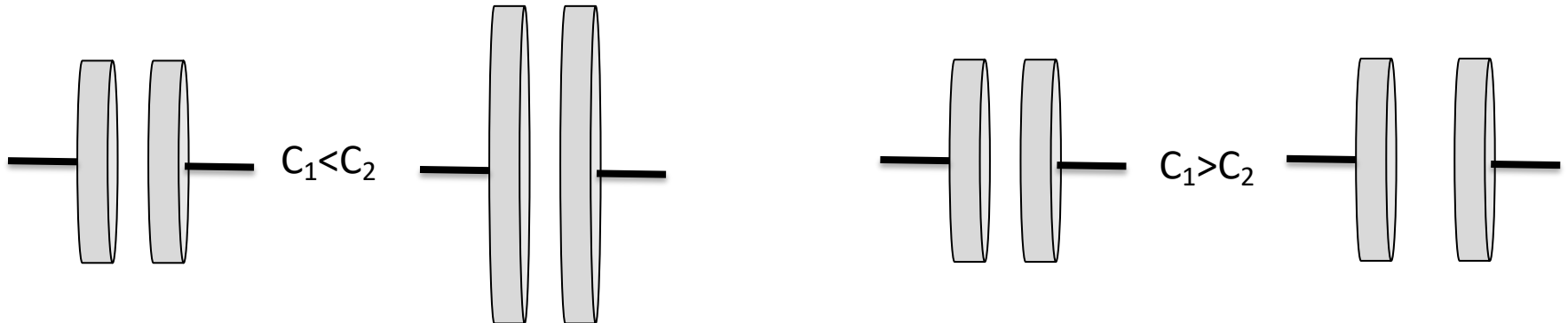

# Capacitance



$$C = \frac{Q}{V}$$

- $C$  is capacitance (in farads, F)
- $Q$  is charge (in coulombs, C)


$$\frac{dV}{dt} = \frac{I}{C}$$

- Remember that  $I = dQ/dt$

# Injecting current across a capacitor

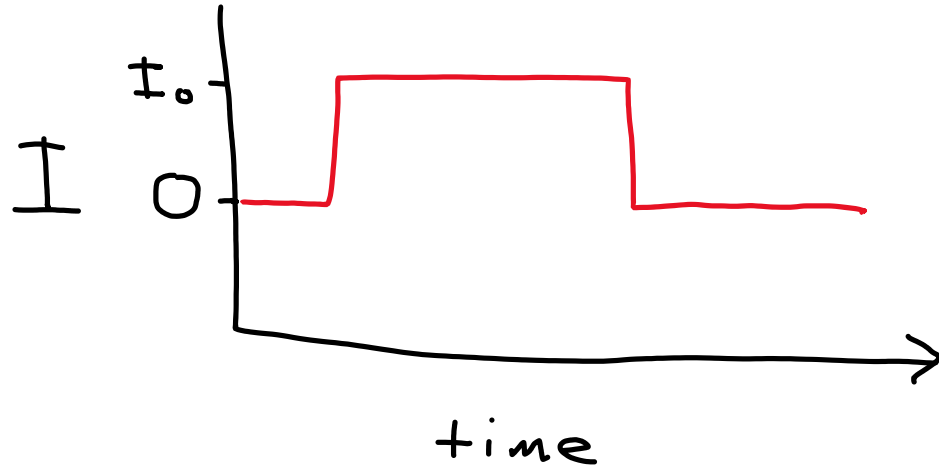
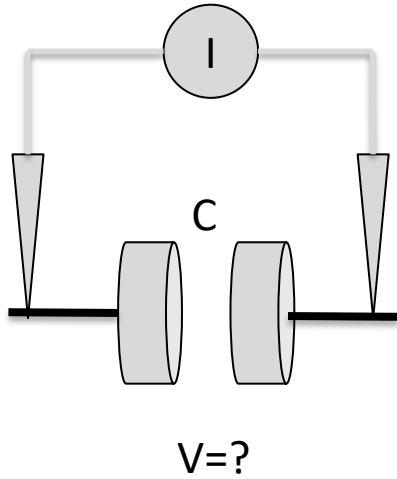


# Injecting current across a capacitor


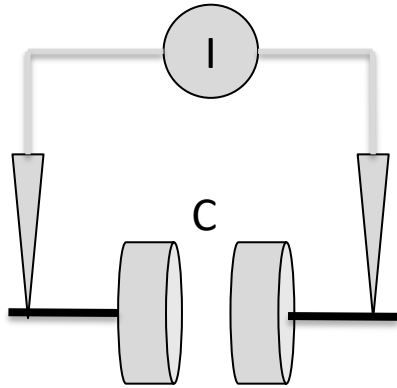


$V=?$


$$dV/dt = I_0/C$$

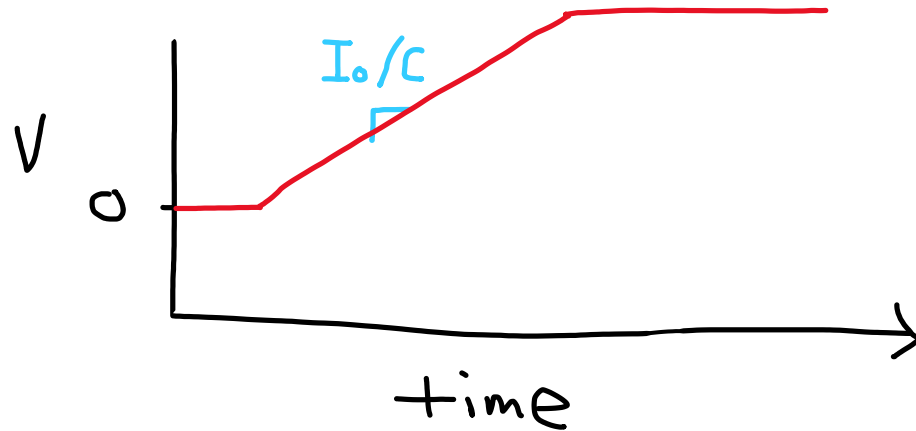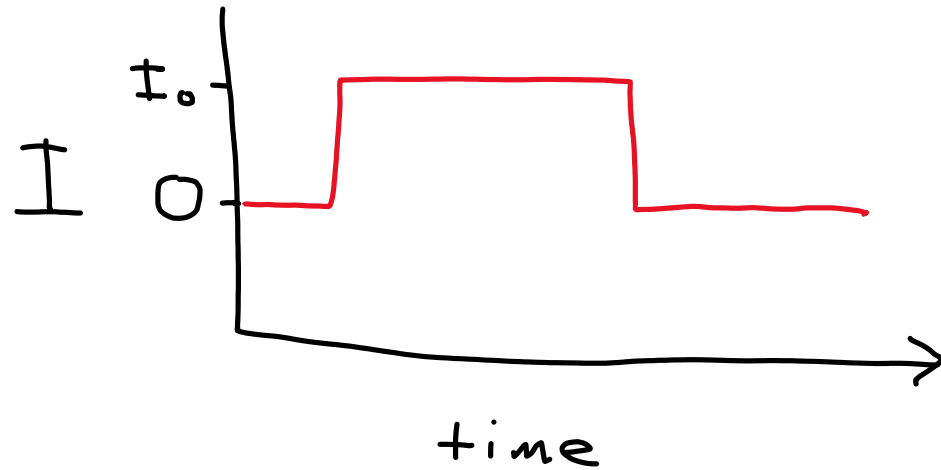

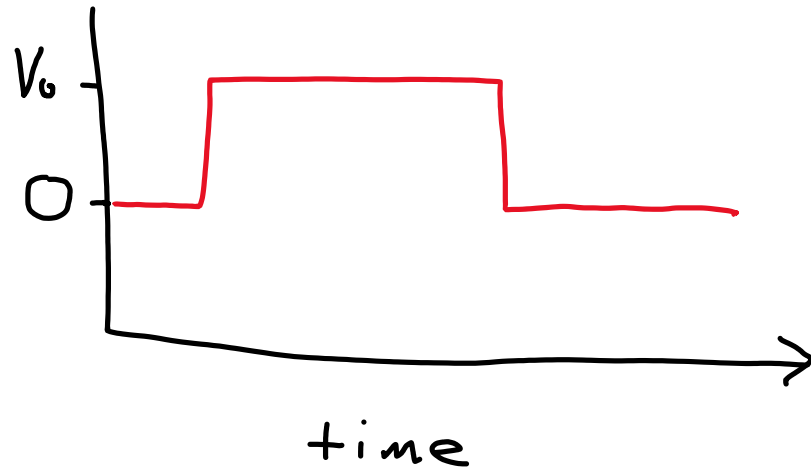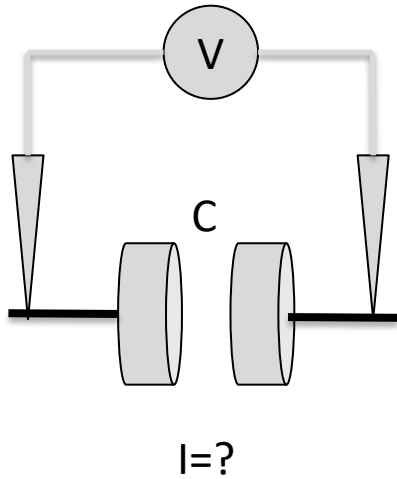
# Clamping the voltage across a capacitor




$$I = C(dV/dt)$$

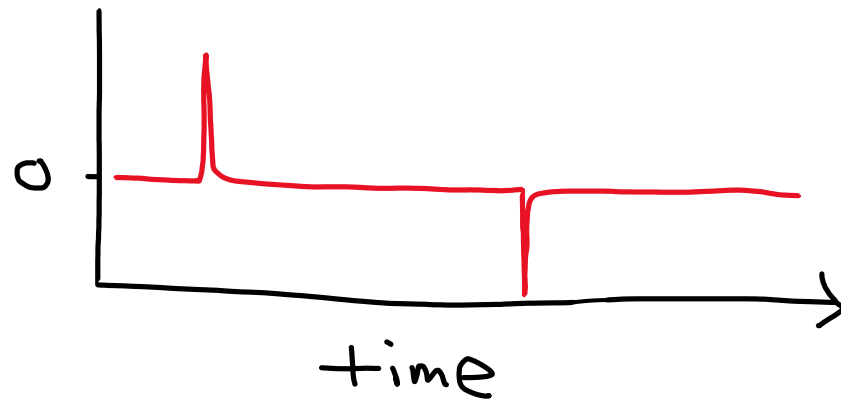


# Lumped resistance and capacitance

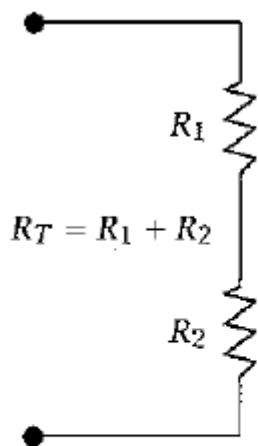


Resistances in Series

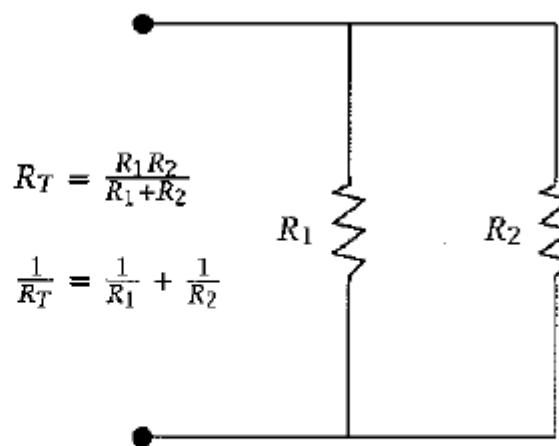

Resistances in Parallel

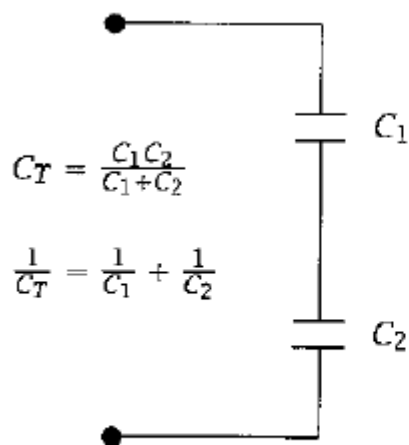


Capacitors in Series

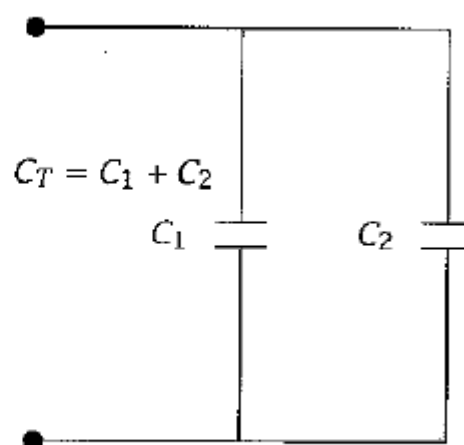


Capacitors in Parallel


# Lumped resistance and capacitance

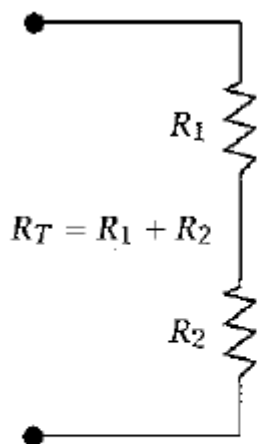


Resistances in Series

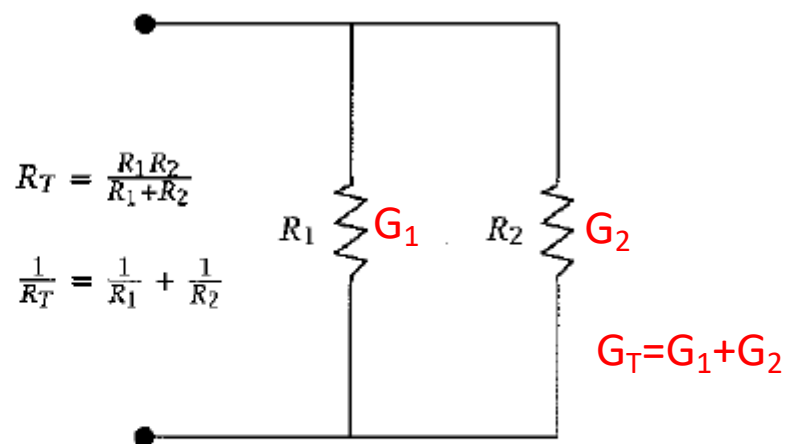

Resistances in Parallel

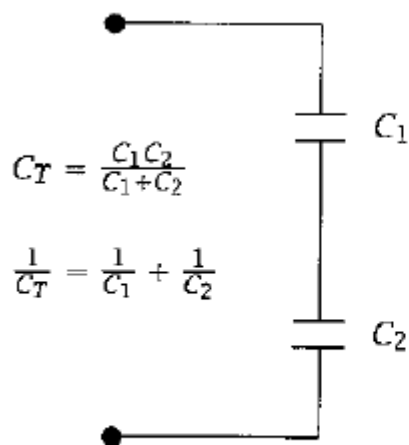


Capacitors in Series

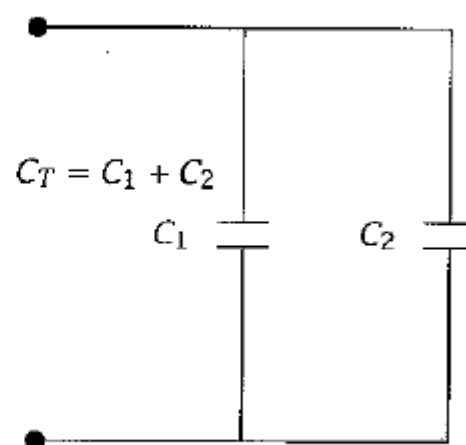


Capacitors in Parallel

# Kirchhoff's Laws

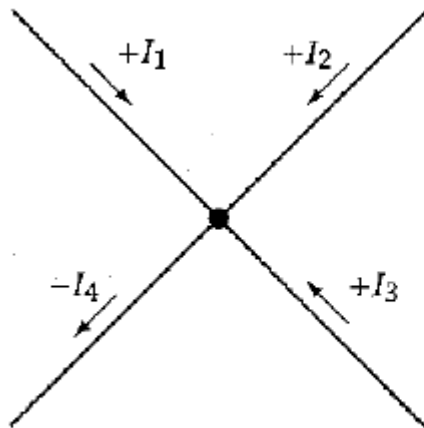1. Current: Conservation of Charge
2. Voltage: Conservation of Current




$$I_1 + I_2 + I_3 - I_4 = 0$$

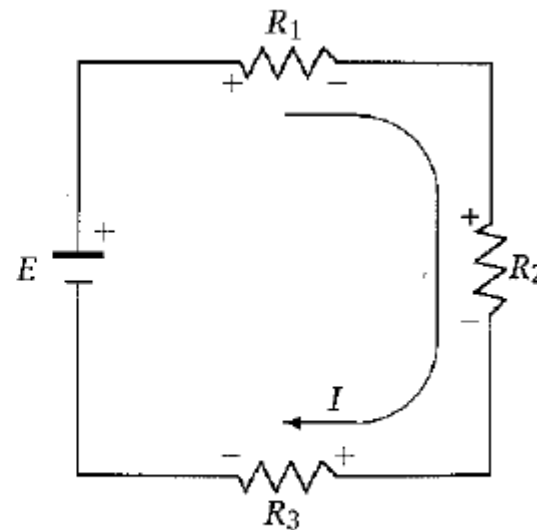


$$E - IR_1 - IR_2 - IR_3 = 0$$



# Resistors and Capacitors

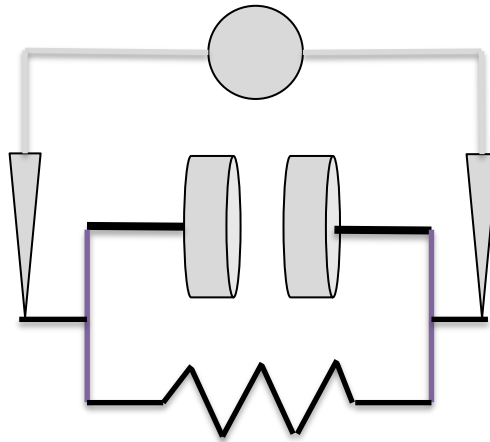

# R and C in parallel (RC circuit)


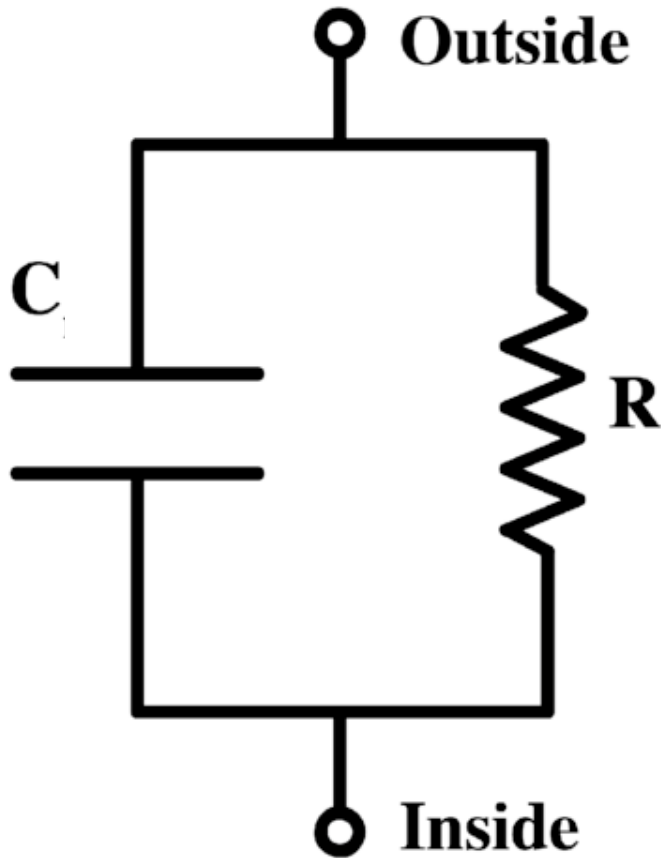


$$I = C \frac{dV}{dt} + \frac{V}{R}$$

# One simple solution: Discharging an RC circuit

$$I = C \frac{dV}{dt} + \frac{V}{R}$$

$V=V_0$  at  $t=0$  and  $I=0$

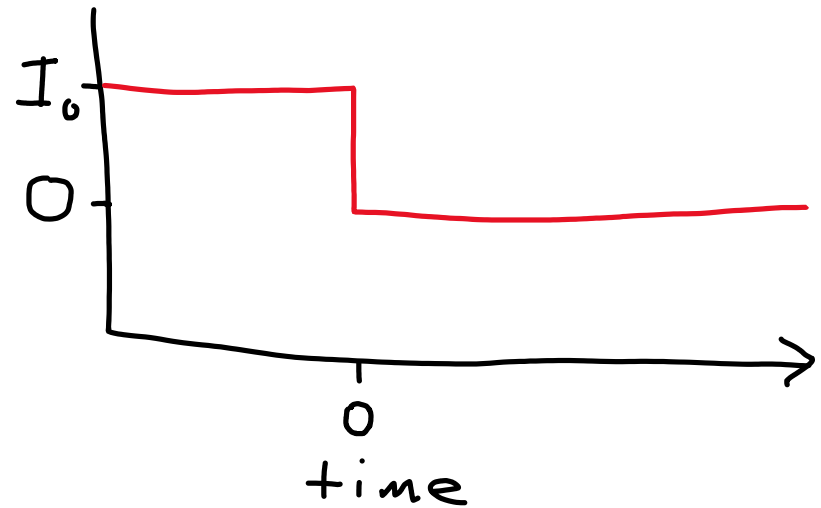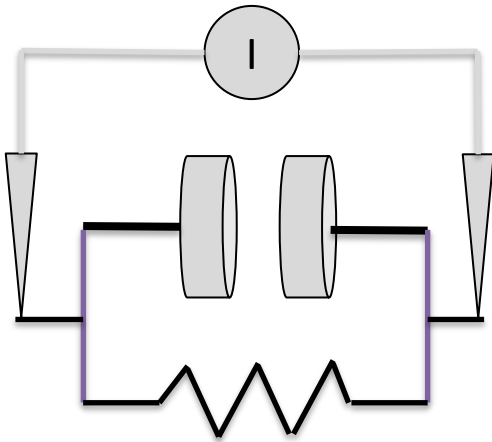

# One simple solution: Discharging an RC circuit

$$I = C \frac{dV}{dt} + \frac{V}{R}$$

$$V=V_0 \text{ at } t=0 \text{ and } I=0$$

$$0 = C \frac{dV}{dt} + \frac{V}{R}$$

$$-\frac{V}{R} = C \frac{dV}{dt}$$

$$-\frac{1}{RC} \int dt = \int \frac{1}{V} dV$$


$$-\frac{1}{RC} t + C = \ln V$$

$$e^{-\frac{t}{RC} + C} = V$$

$$V = V_0 e^{-\frac{t}{RC}}$$

# One simple solution: Discharging an RC circuit



$$V = V_0 e^{-\frac{t}{RC}}$$

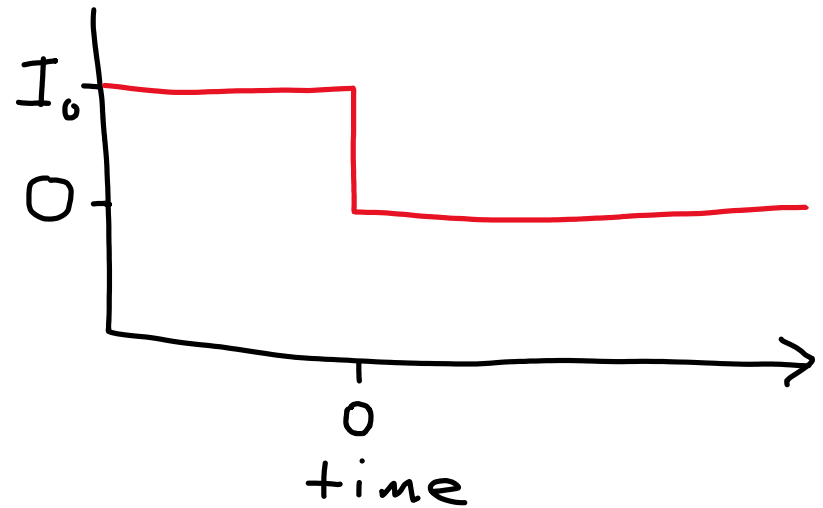
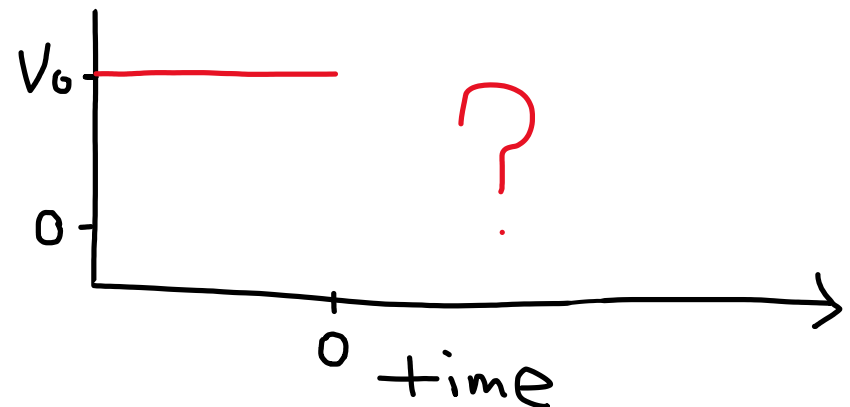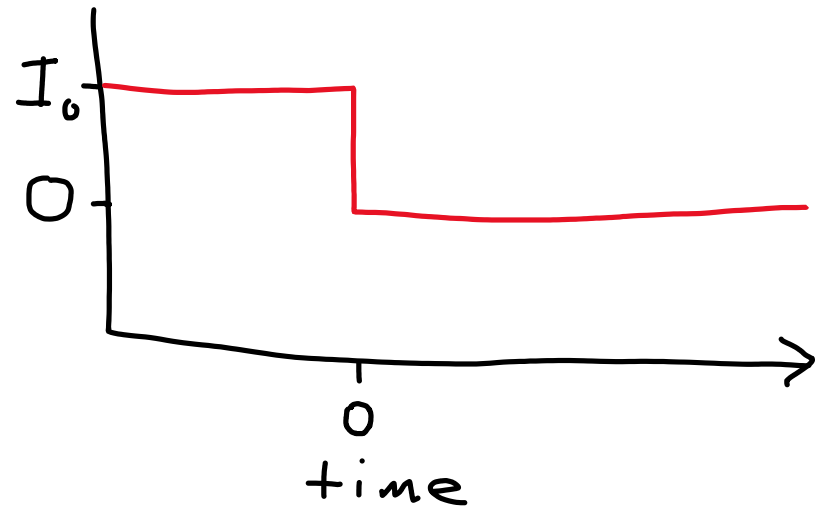
# One simple solution: Discharging an RC circuit

$$V = V_0 e^{-\frac{t}{RC}}$$


- When  $t=0$ ,  $V=V_0$
- When  $t=RC=\tau_m$   
 $V = V_0 e^{-1} = 0.368V_0$


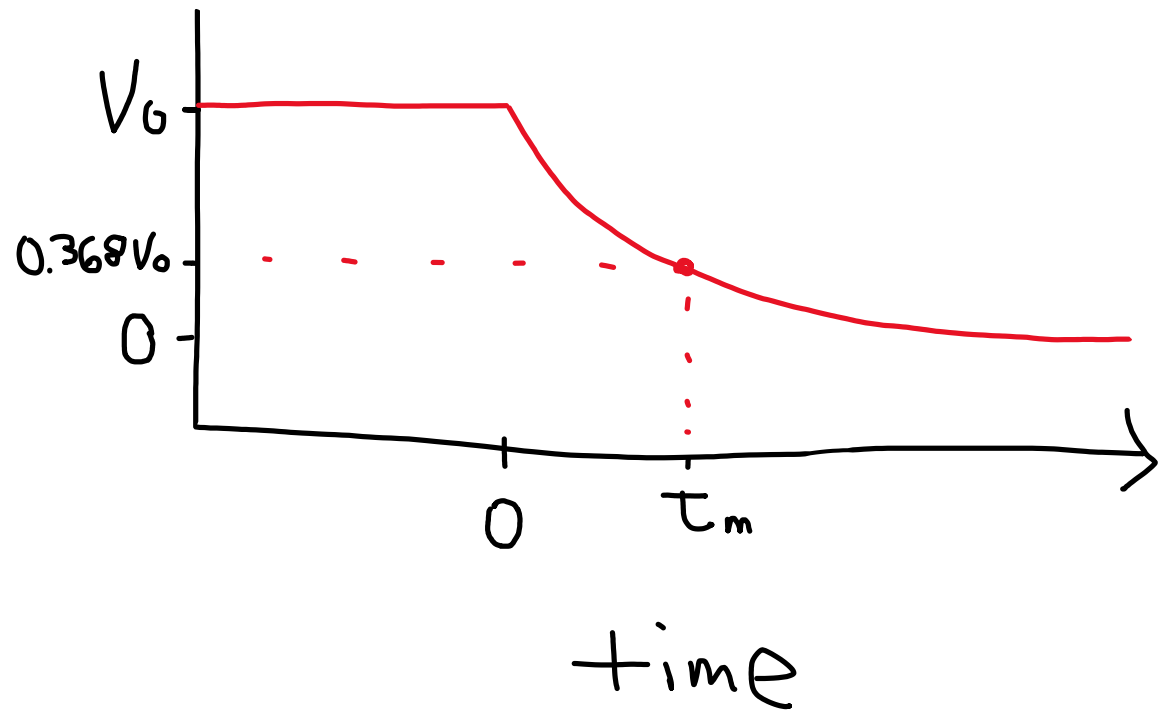
# One simple solution: Discharging an RC circuit

$$V = V_0 e^{-\frac{t}{RC}}$$


- When  $t=0$ ,  $V=V_0$
- When  $t=RC=\tau_m$   
 $V = V_0 e^{-1} = 0.368V_0$


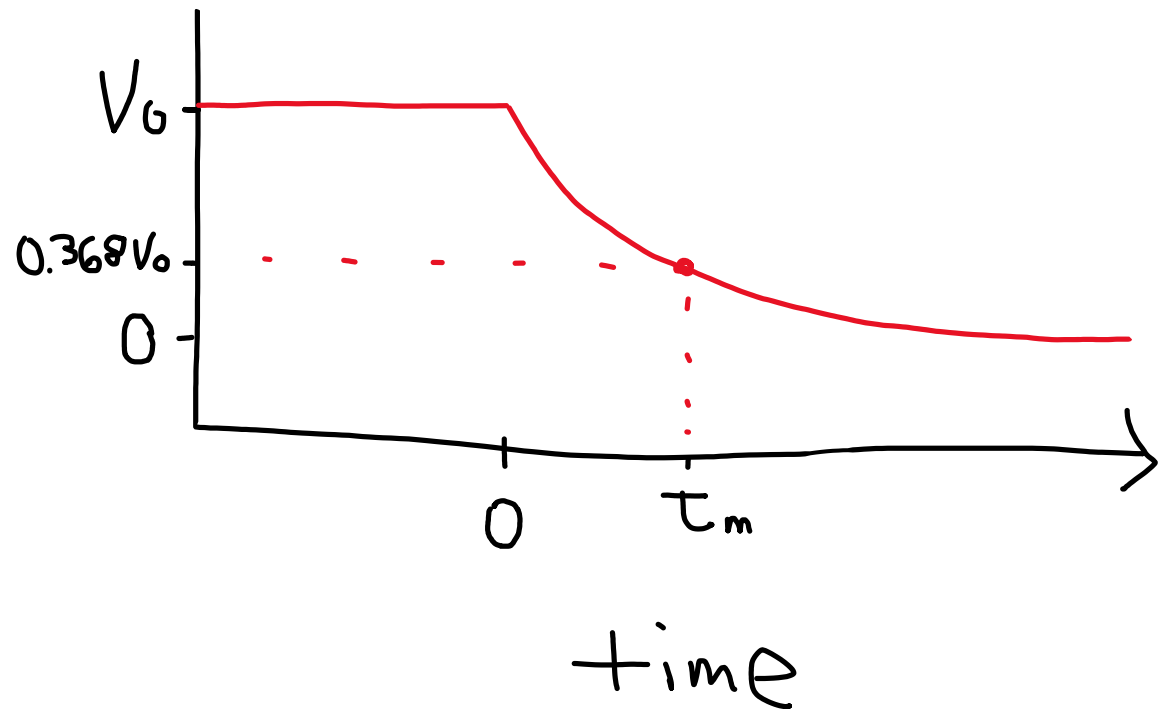
# One simple solution: Discharging an RC circuit

$$V = V_0 e^{-\frac{t}{RC}}$$

- When  $t=0$ ,  $V=V_0$
- When  $t=RC=\tau_m$   
 $V = V_0 e^{-1} = 0.368V_0$



The time constant  $\tau_m = RC$


Voltage follows an exponential decay.

Every  $\tau_m$  seconds the voltage becomes  $1/e$  (0.368) of its previous value.



# One simple solution: Charging an RC circuit



$$V = V_0(1 - e^{-\frac{t}{RC}})$$

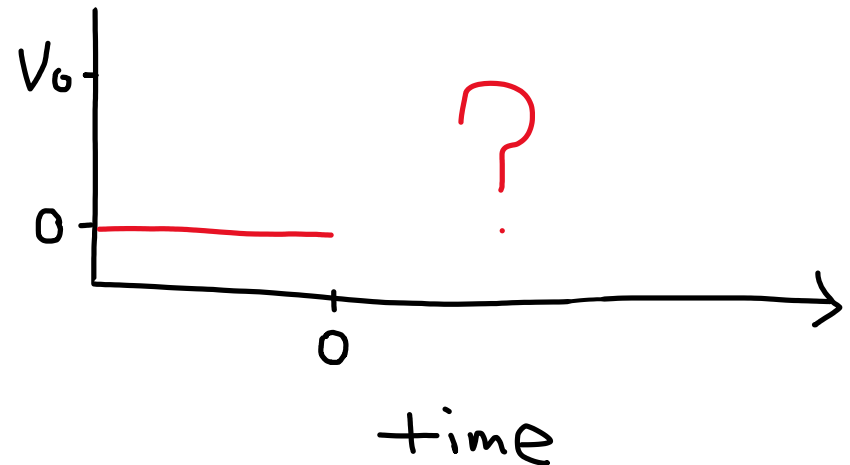
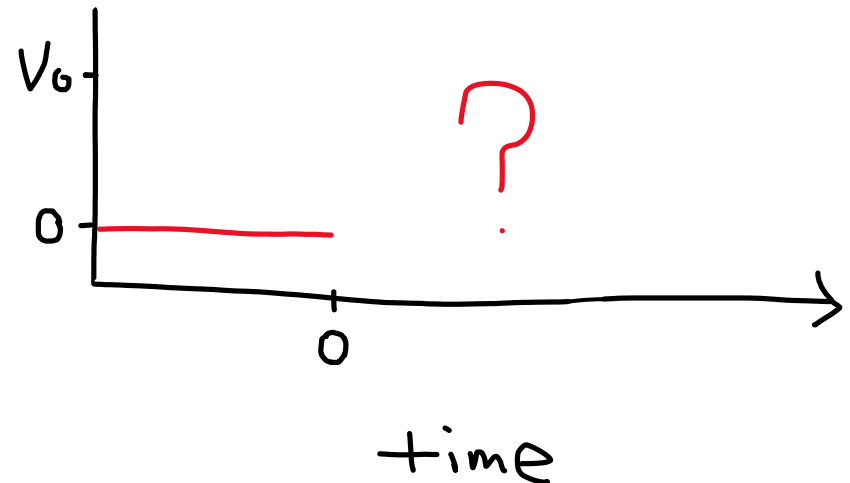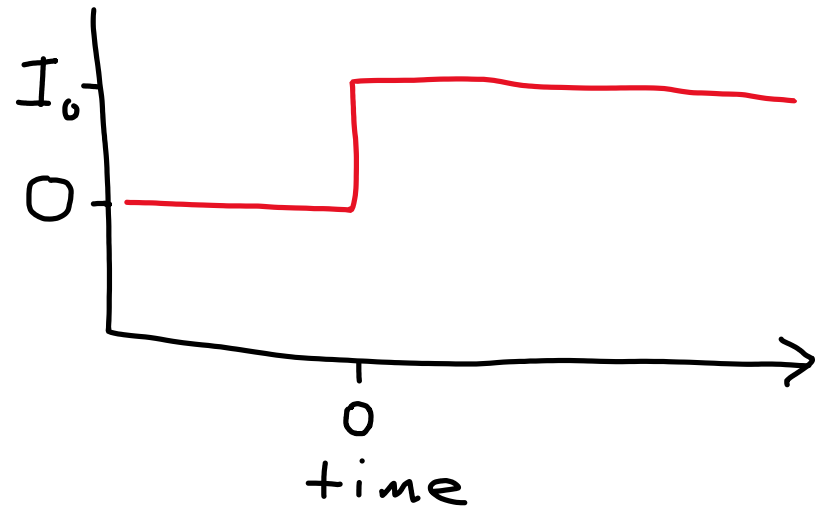
# One simple solution: Charging an RC circuit

$$V = V_0(1 - e^{-\frac{t}{RC}})$$



- When  $t=0$ ,  $V=0$
- When  $t=RC=\tau_m$   
 $V = V_0(1 - e^{-1}) = 0.632V_0$


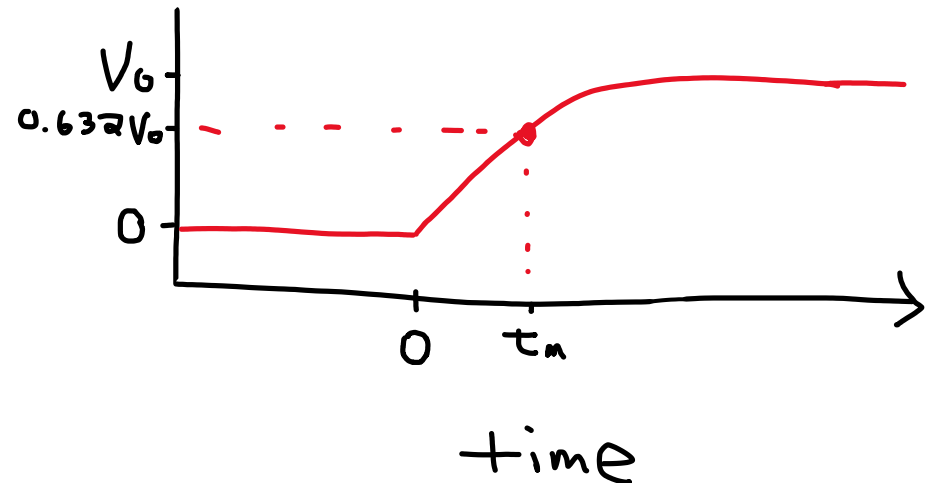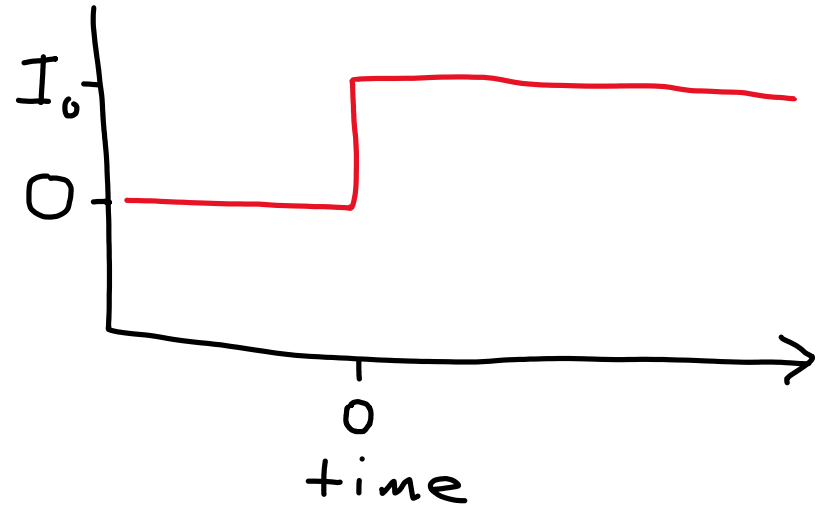
# One simple solution: Charging an RC circuit

$$V = V_0(1 - e^{-\frac{t}{RC}})$$


- When  $t=0$ ,  $V=0$
- When  $t=RC=\tau_m$   
 $V = V_0(1 - e^{-1}) = 0.632V_0$



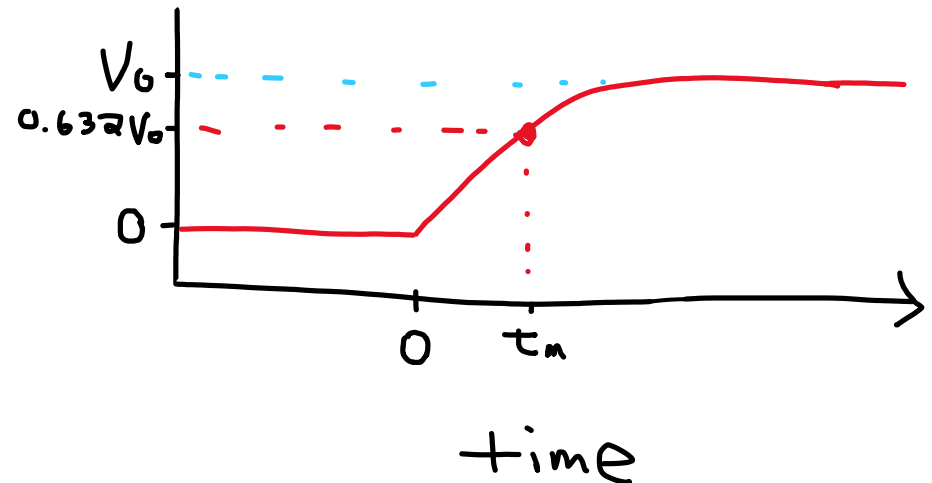
# One simple solution: Charging an RC circuit

$$V = V_0(1 - e^{-\frac{t}{RC}})$$



- When  $t=0$ ,  $V=0$
- When  $t=RC=\tau_m$   
 $V = V_0(1 - e^{-1}) = 0.632V_0$
- When  $t \gg 0$  (steady state)  
 $V = V_0 = I_0 R$



# R and C in parallel (RC circuit)

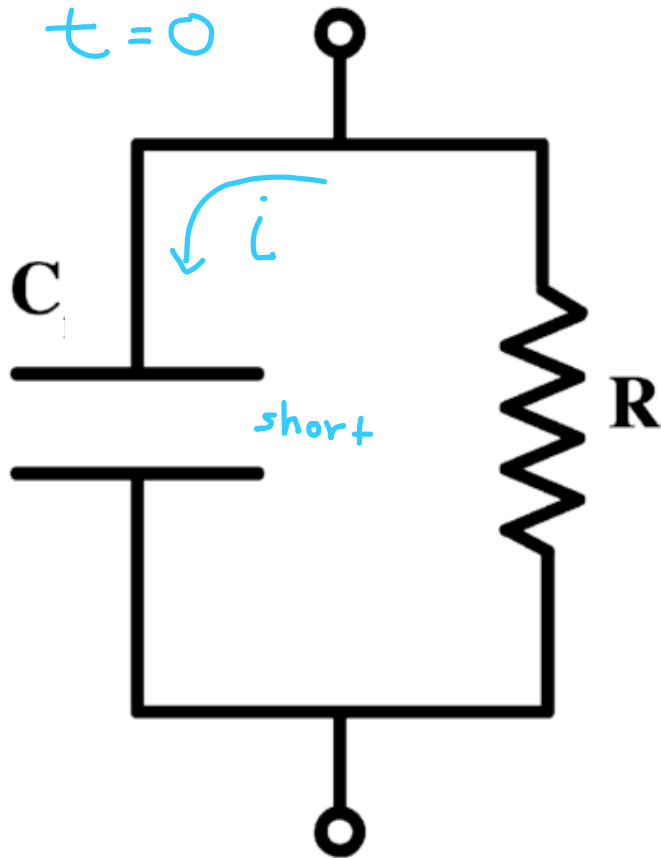


# R and C in parallel (RC circuit)

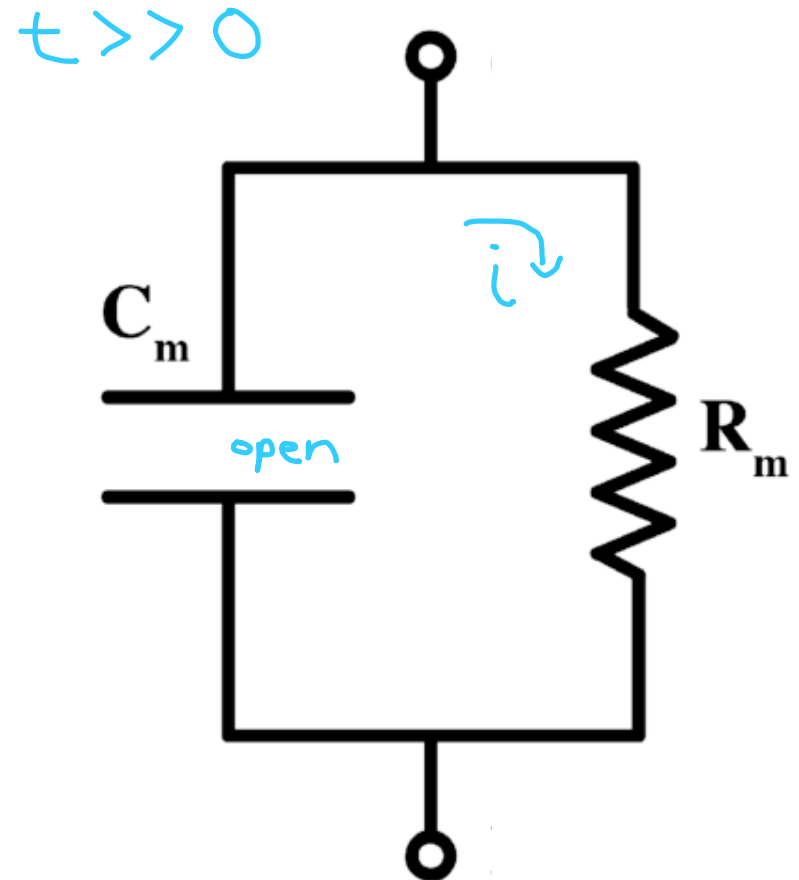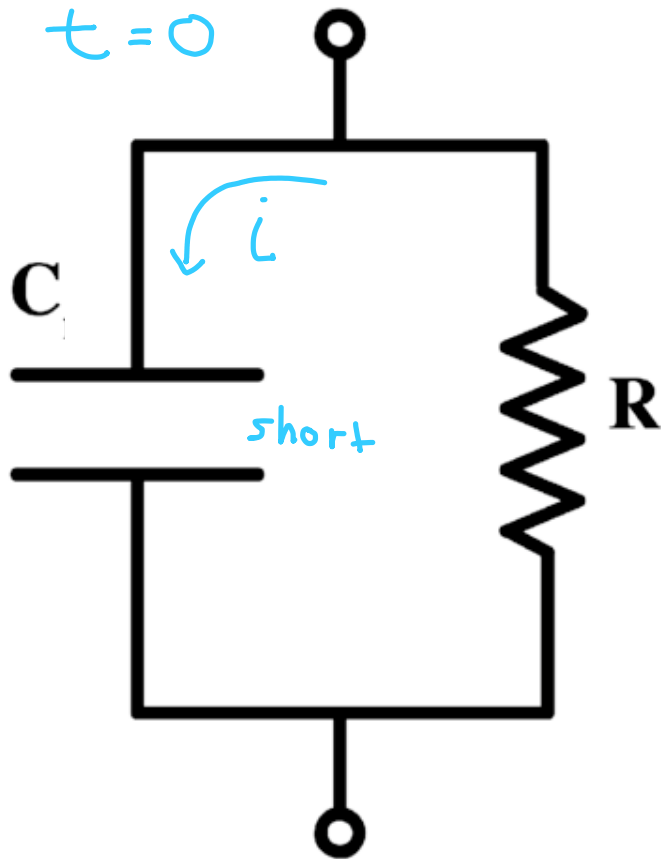


# Acquiring neural data






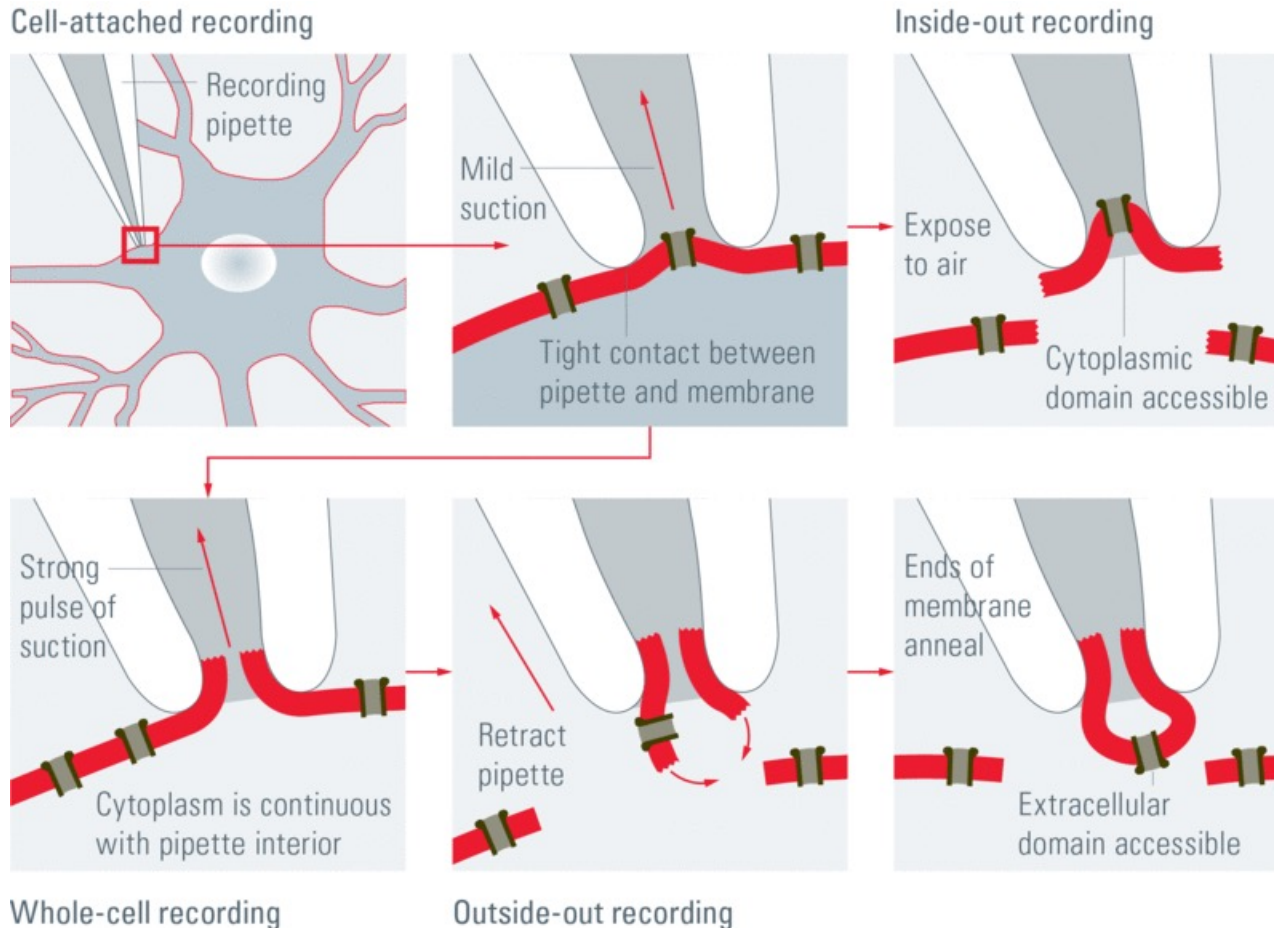
## Whole-cell, patch-clamp electrophysiology



# Patching neurons in vitro

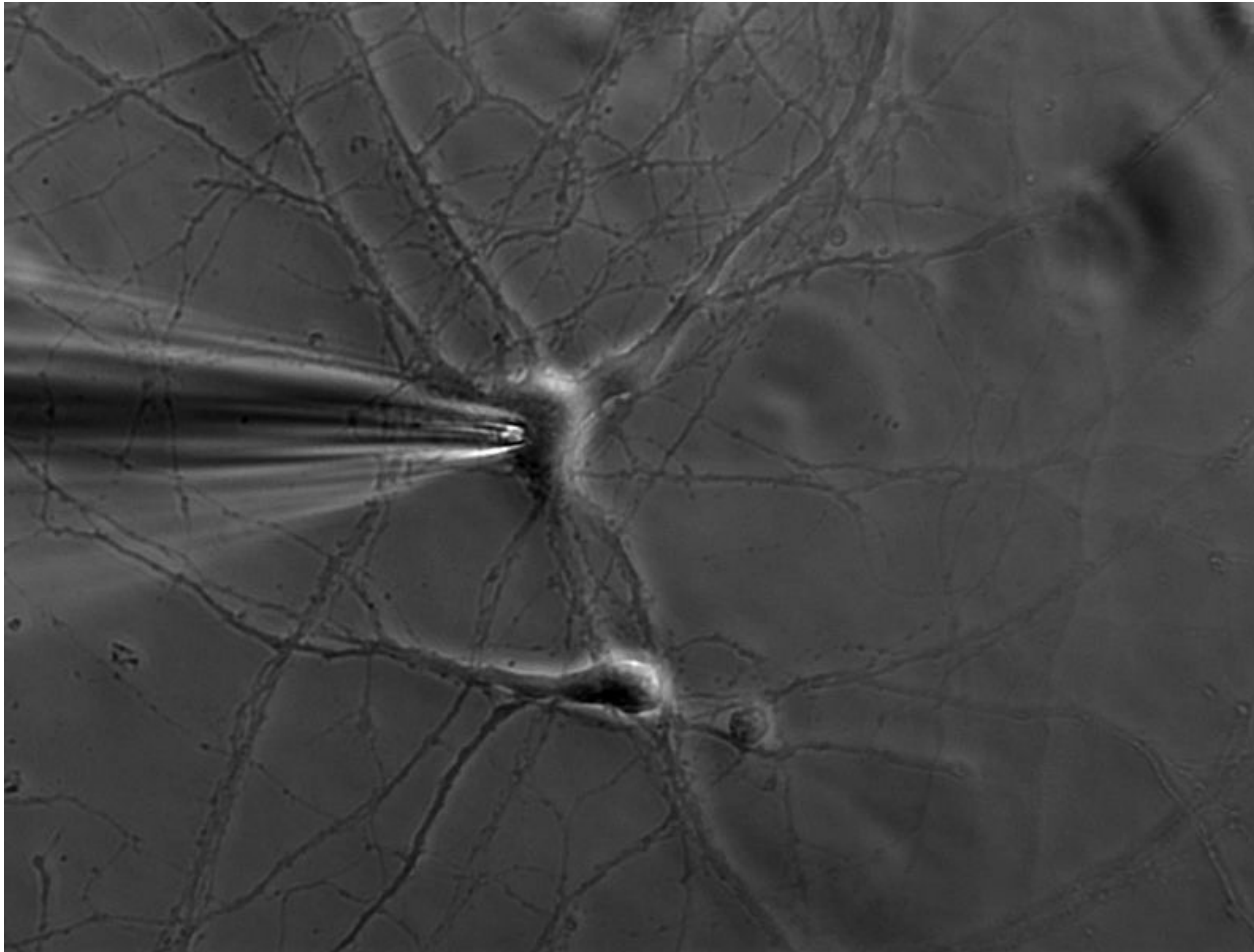




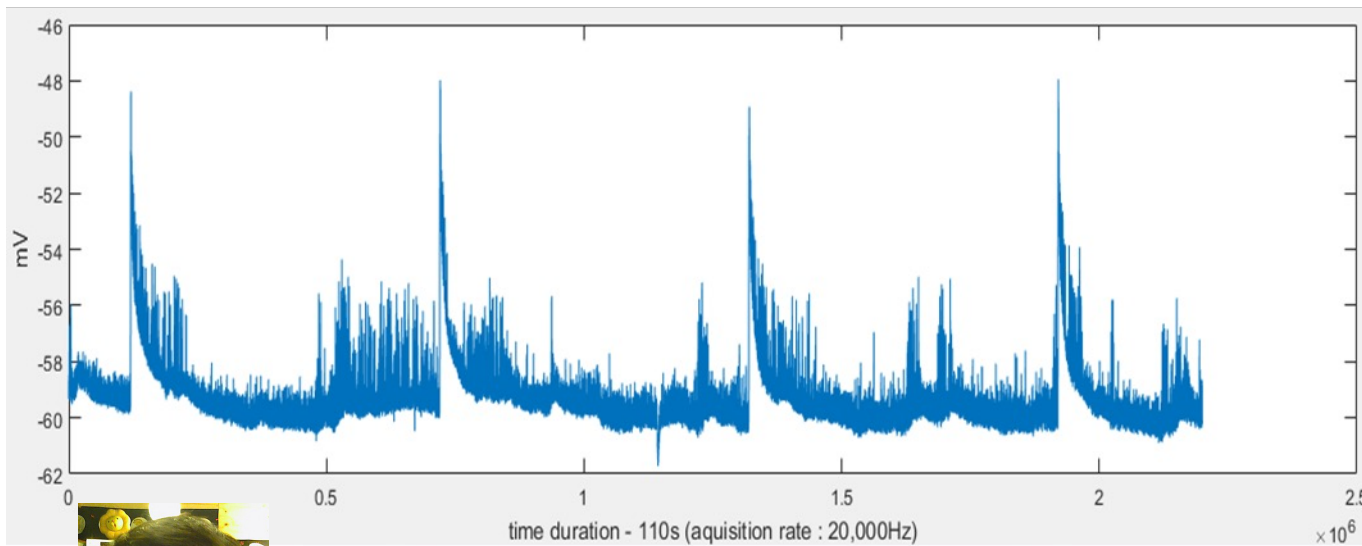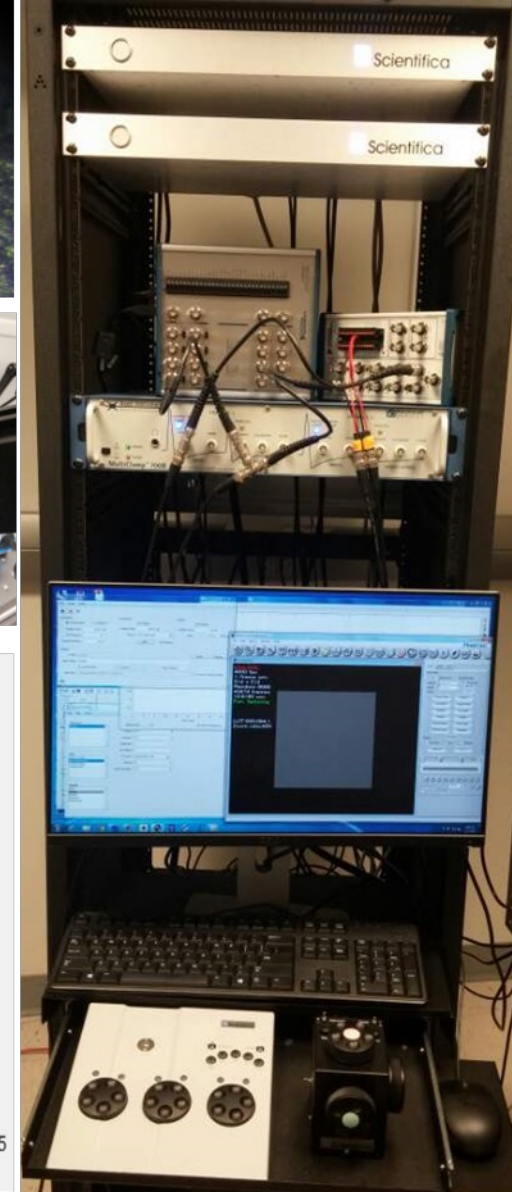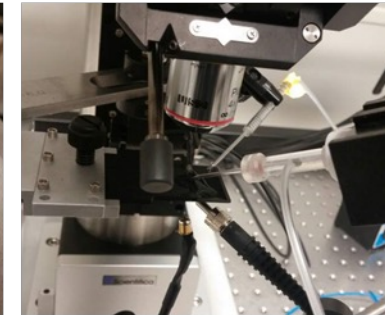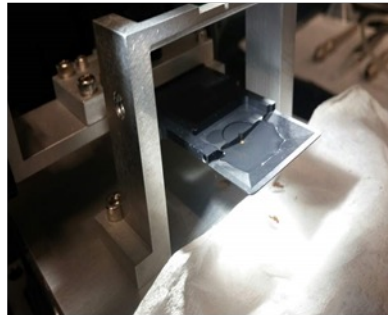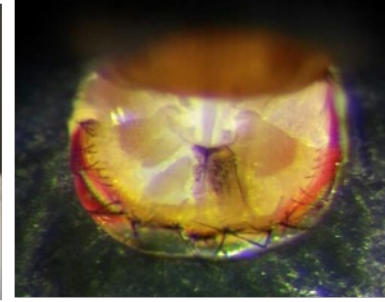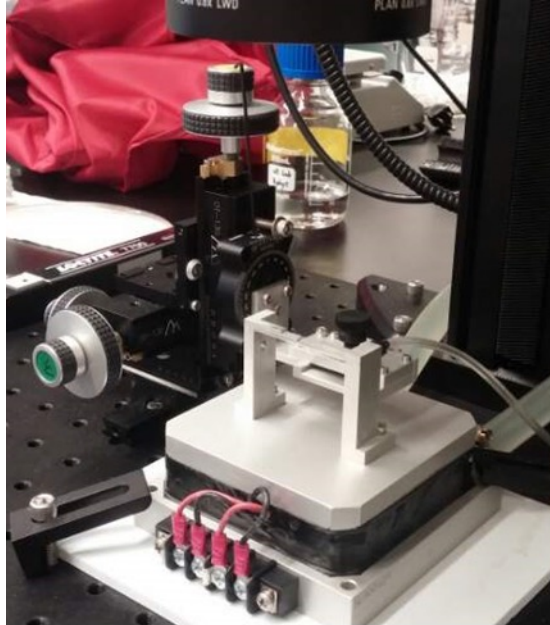

HyoJong Jang


# Patching neurons in vivo
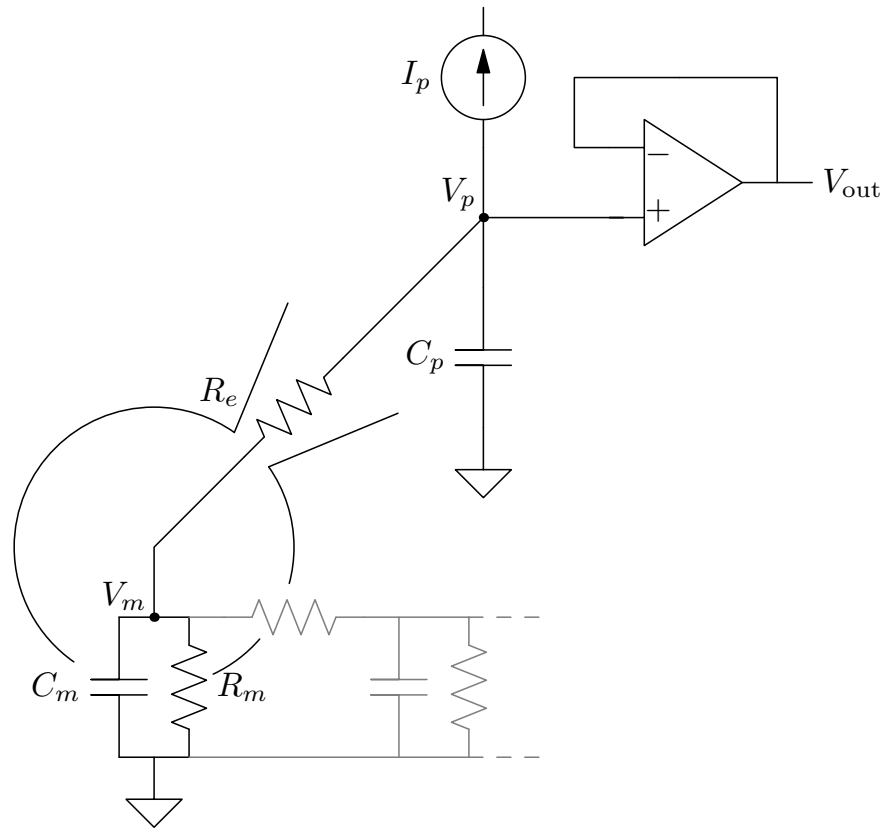
# Current clamp uses a “voltage follower” op-amp configuration



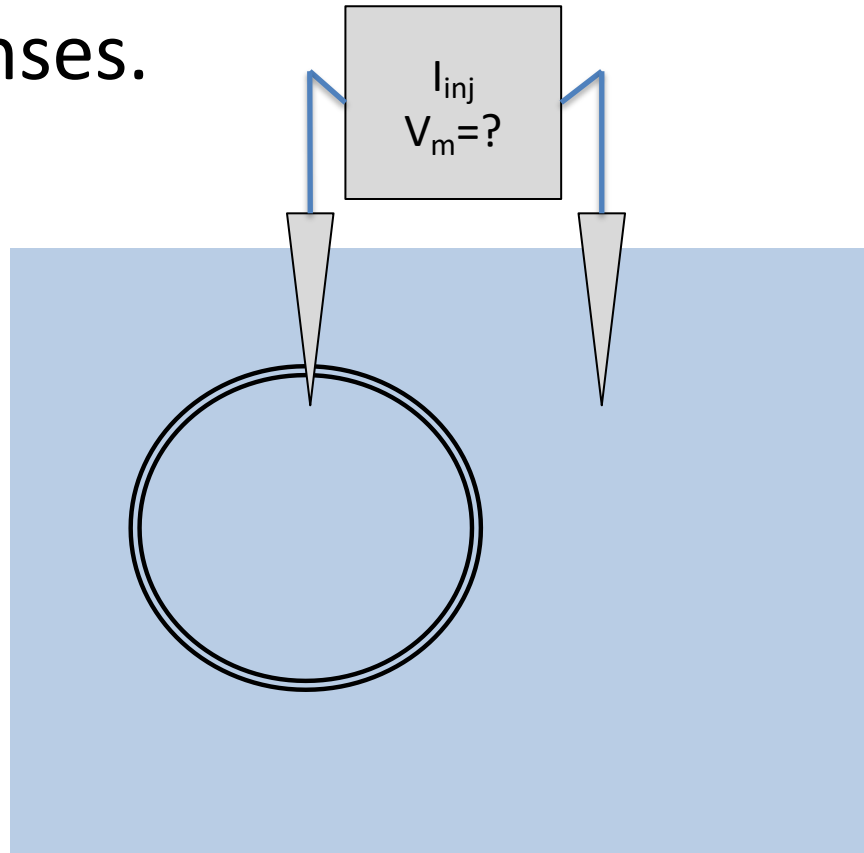
# Acquiring neural data


- Current clamp – not really “clamping” but actually just injecting current and measuring voltage responses.




# Real current injection experiments

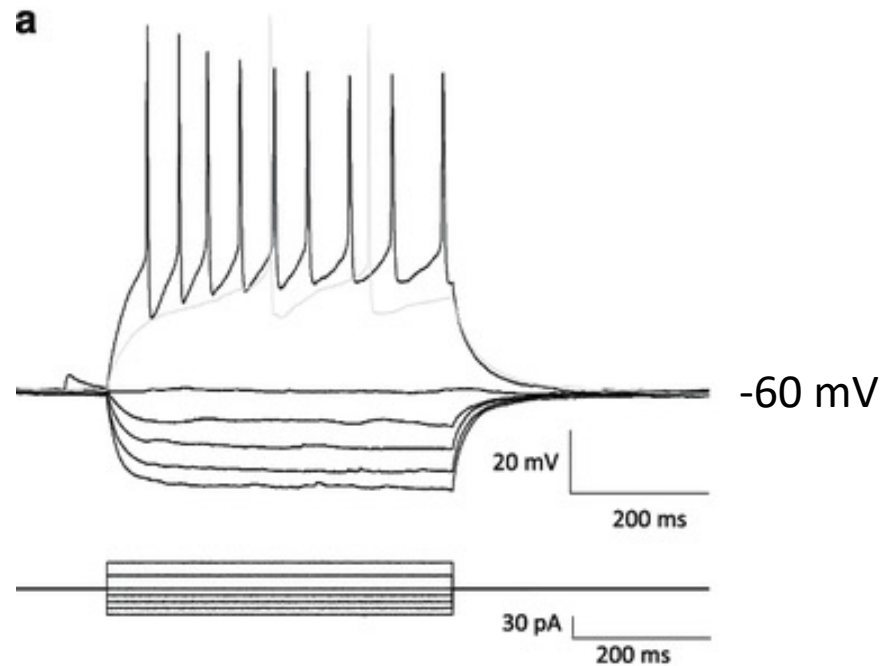


# Real current injection experiments

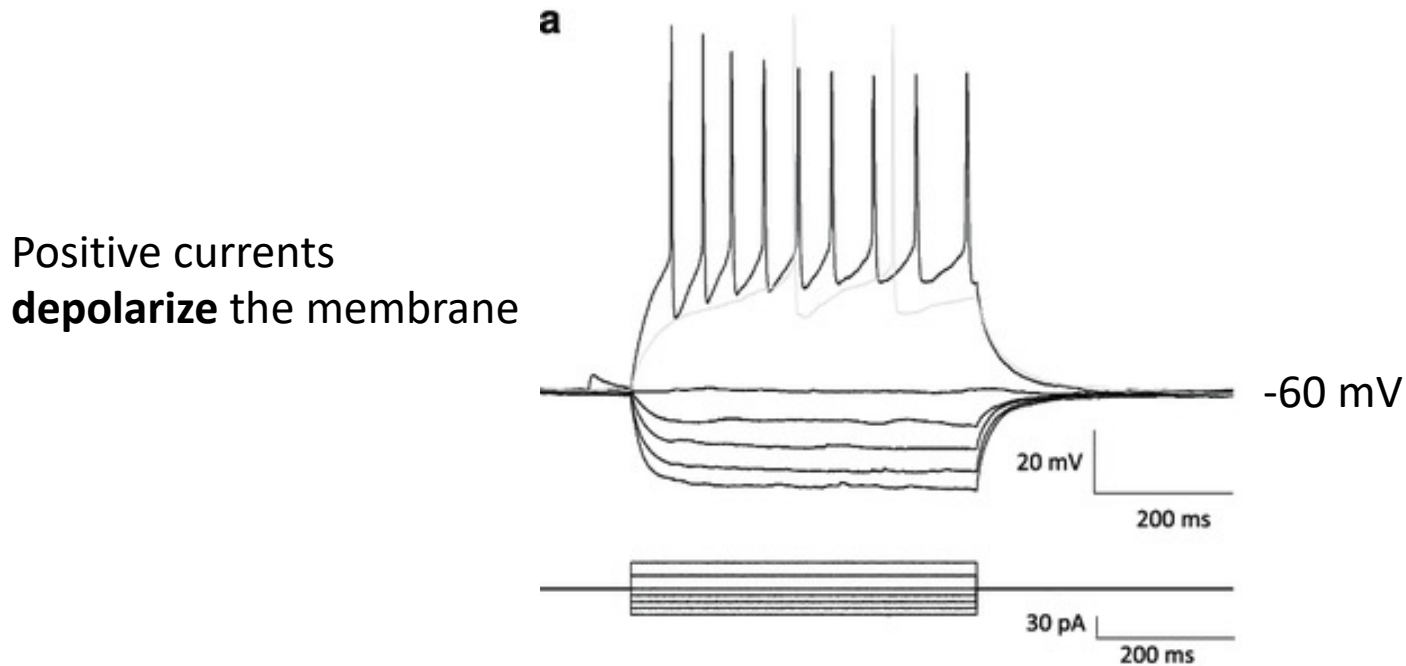

# Real current injection experiments

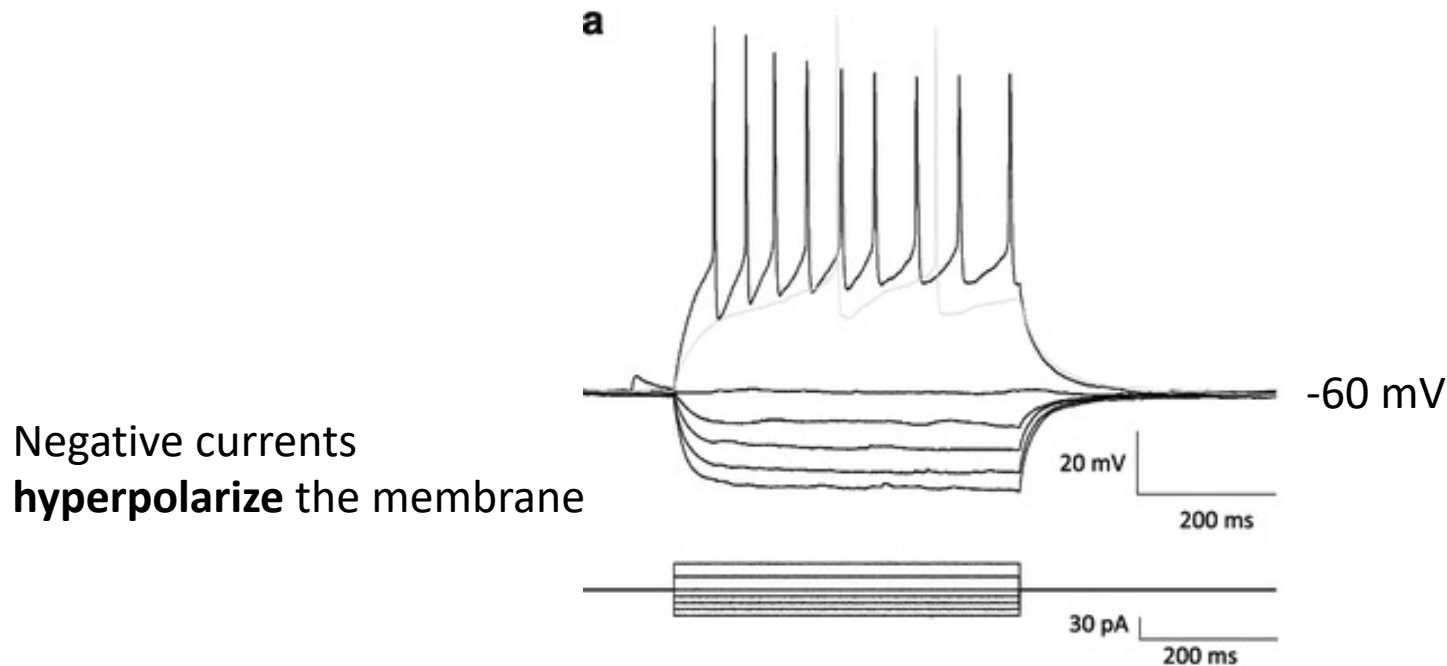

# Real current injection experiments

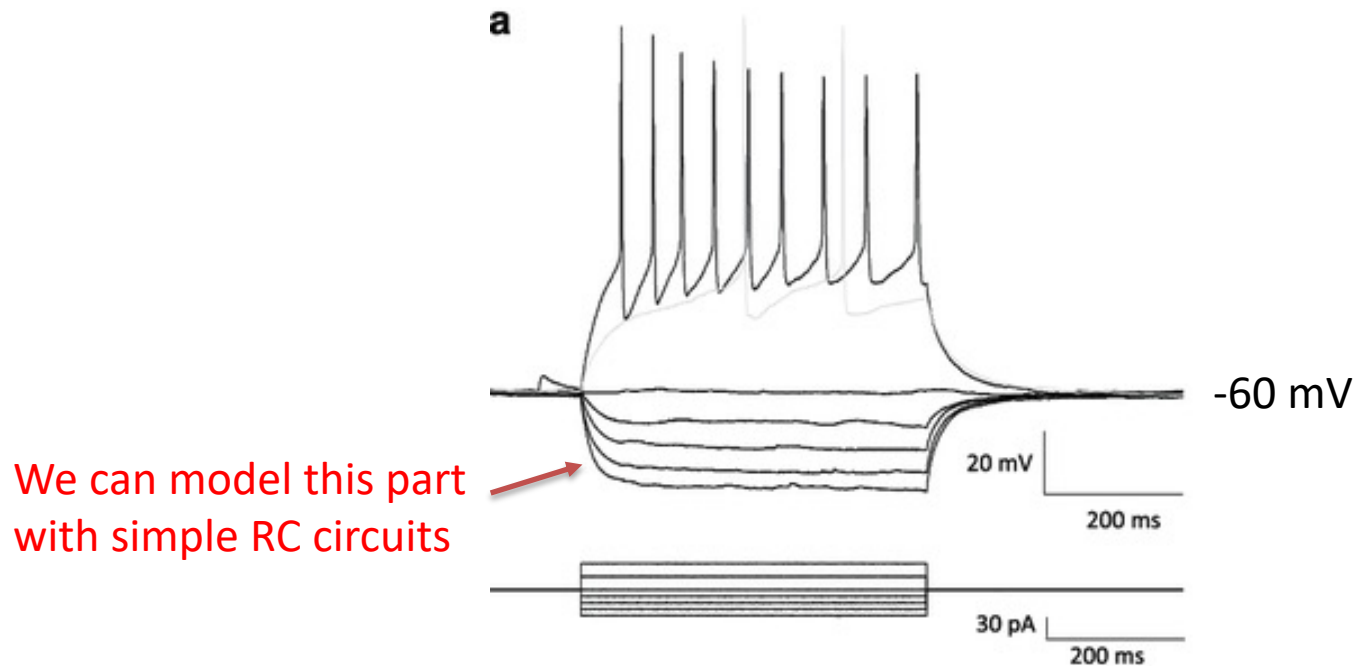

# Membrane properties

Neurons have membrane properties that impact electrical signaling:

1. Ions flow across the membrane...

Membrane resistance,  $R_m$

2. Flow of ions induces charge separation...


Membrane capacitance,  $C_m$

3. Ions flow down the length of a process...


Axial membrane resistance,  $R_a$




# The membrane is a capacitor...

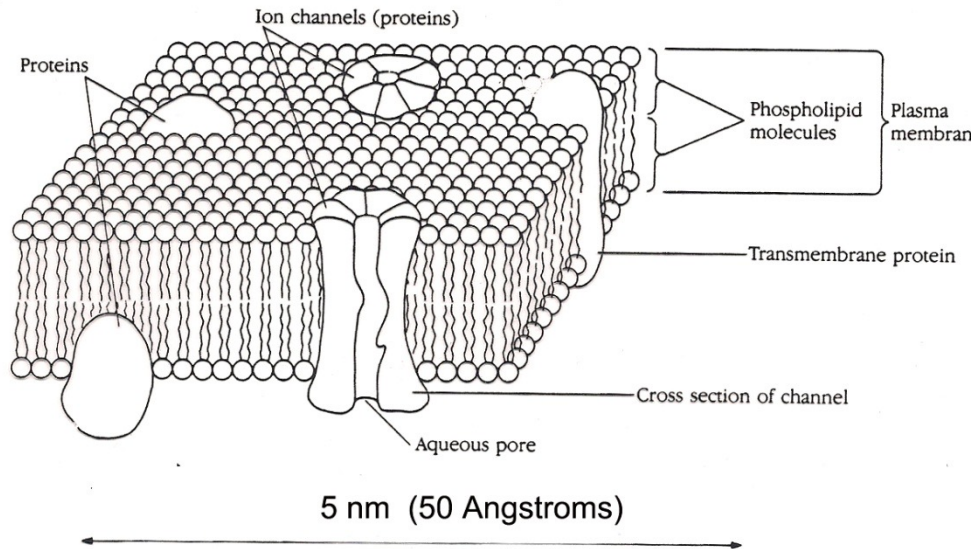

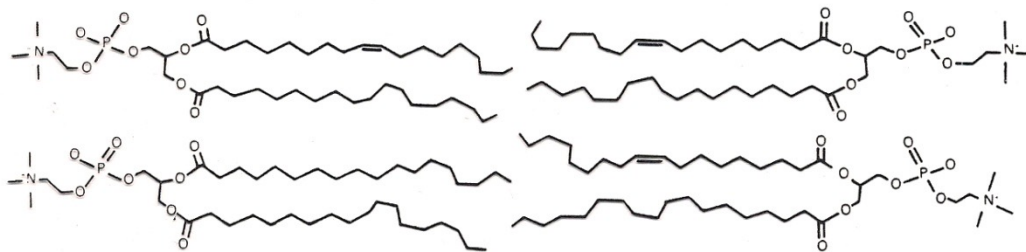- The cell membrane is an insulator surrounded by a conductor (saline).




# ... and a resistor

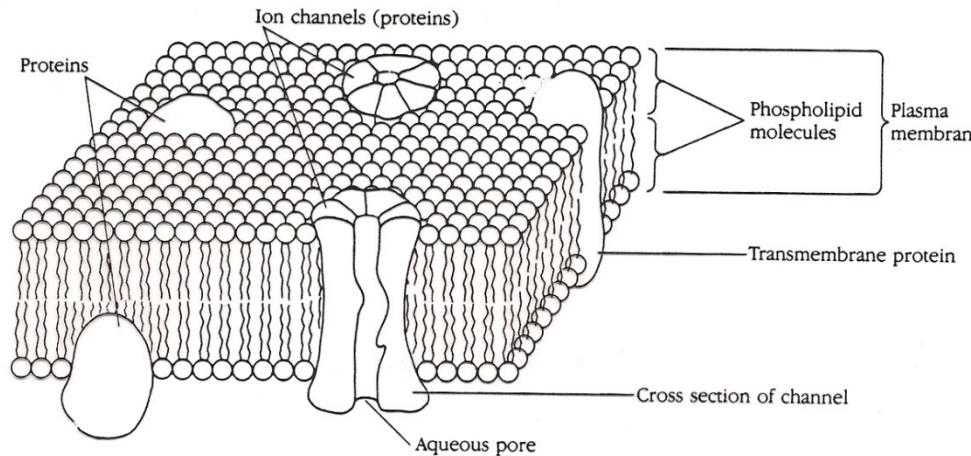


- Membrane resistance is set by channels embedded in the membrane. (Without channels, the resistance would be extremely high, and there would be no way for current to flow across the membrane)
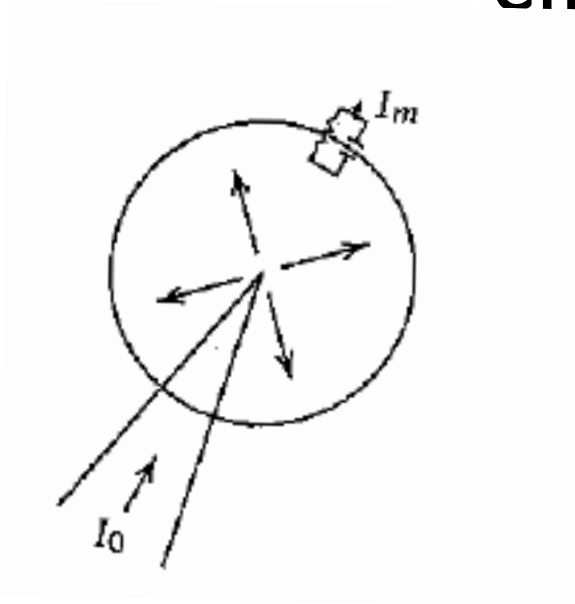
# Consider the cell membrane as an RC circuit




- Current injected will distribute uniformly across the surface
- Current across a unit of area is the **sum** of the current through the capacitor and the resistor
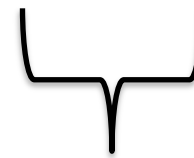
$$I_m = C_m \frac{dV_m}{dt} + \frac{V_m}{R_m}$$



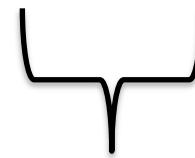Current from  
the membrane  
capacitance



Current from  
the membrane  
resistance

Finite step of current for a time interval  $0 < T < t$ , across the membrane:

$$I(t) = C_m \frac{dV_m}{dt} + \frac{V_m}{R_m}$$

$$I(t) = \begin{cases} 0 & t < 0 \\ I_{inj} & 0 < t < T \\ 0 & t > T \end{cases}$$

$$V_m = \begin{cases} 0 & t < 0 \\ I_m R_m \left( 1 - e^{-\frac{t}{\tau_m}} \right) & 0 < t < T \\ I_m R_m e^{-\frac{t}{\tau_m}} & t > T \end{cases}$$


Finite step of current for a time interval  $0 < T < t$ , across a unit of area of membrane:

$$I(t) = C_m \frac{dV_m}{dt} + \frac{V_m}{R_m}$$

$$I(t) = \begin{cases} 0 & t < 0 \\ I_{inj} & 0 < t < T \\ 0 & t > T \end{cases}$$

$$V_m = \begin{cases} 0 & t < 0 \\ I_m R_m \left( 1 - e^{-\frac{t}{\tau_m}} \right) & 0 < t < T \\ I_m R_m e^{-\frac{t}{\tau_m}} & t > T \end{cases}$$

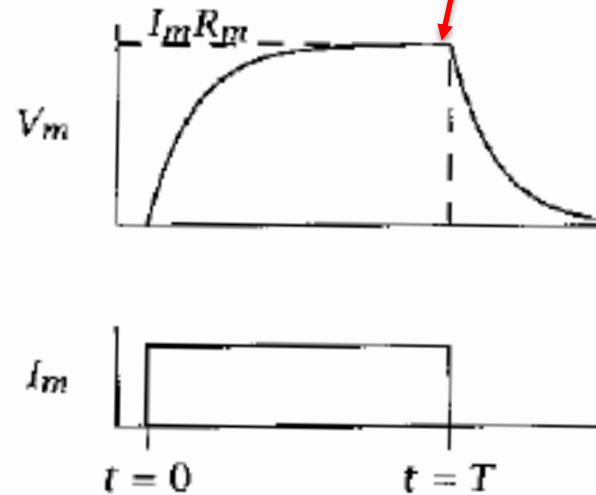Here,  $I_m = I_{inj}$  and  $V_{ss} = I_{inj} R_m$




# Adding the resting membrane potential


- Our RC model takes into consideration the membrane resistance and capacitance, but how do we incorporate the resting membrane potential?
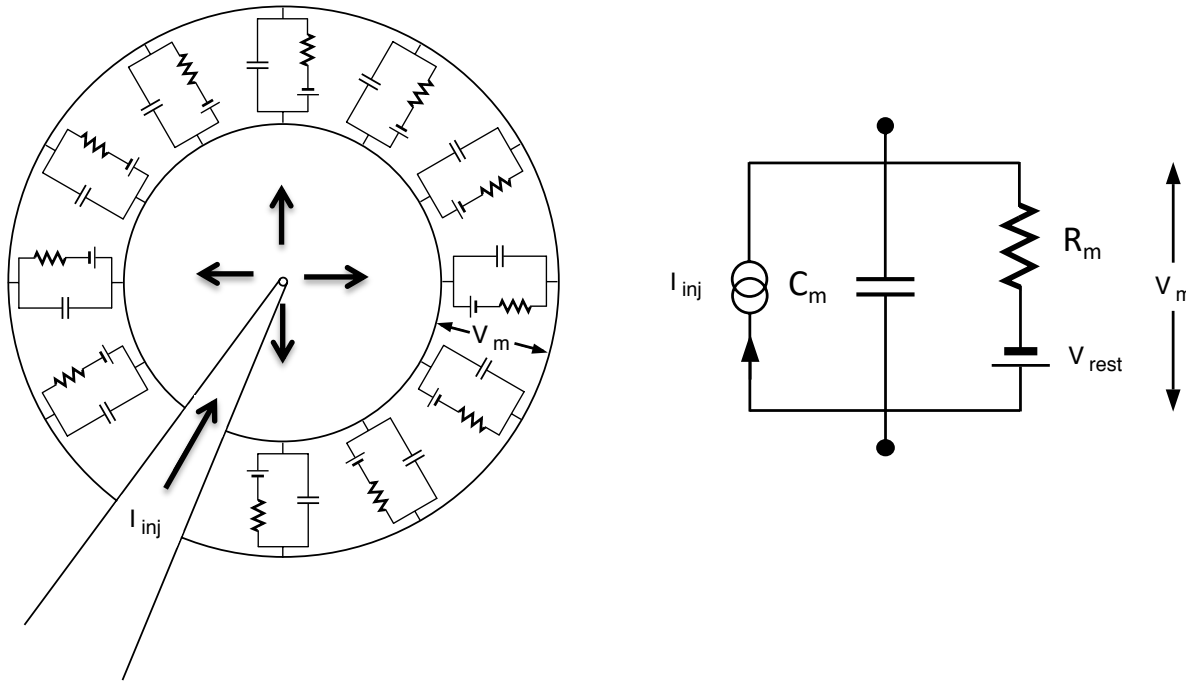
# Adding a voltage source to the RC model

- Model the entire neuron using the RC circuit model
- Use a voltage source to account for  $V_{\text{rest}}$




# Current equation for isopotential cell

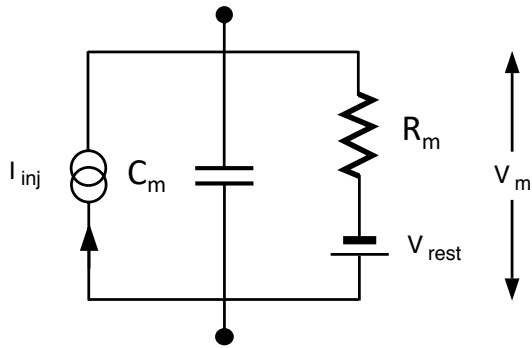

$$I_{inj} = C_m \frac{dV_m}{dt} + \frac{(V_m - V_{rest})}{R_m}$$


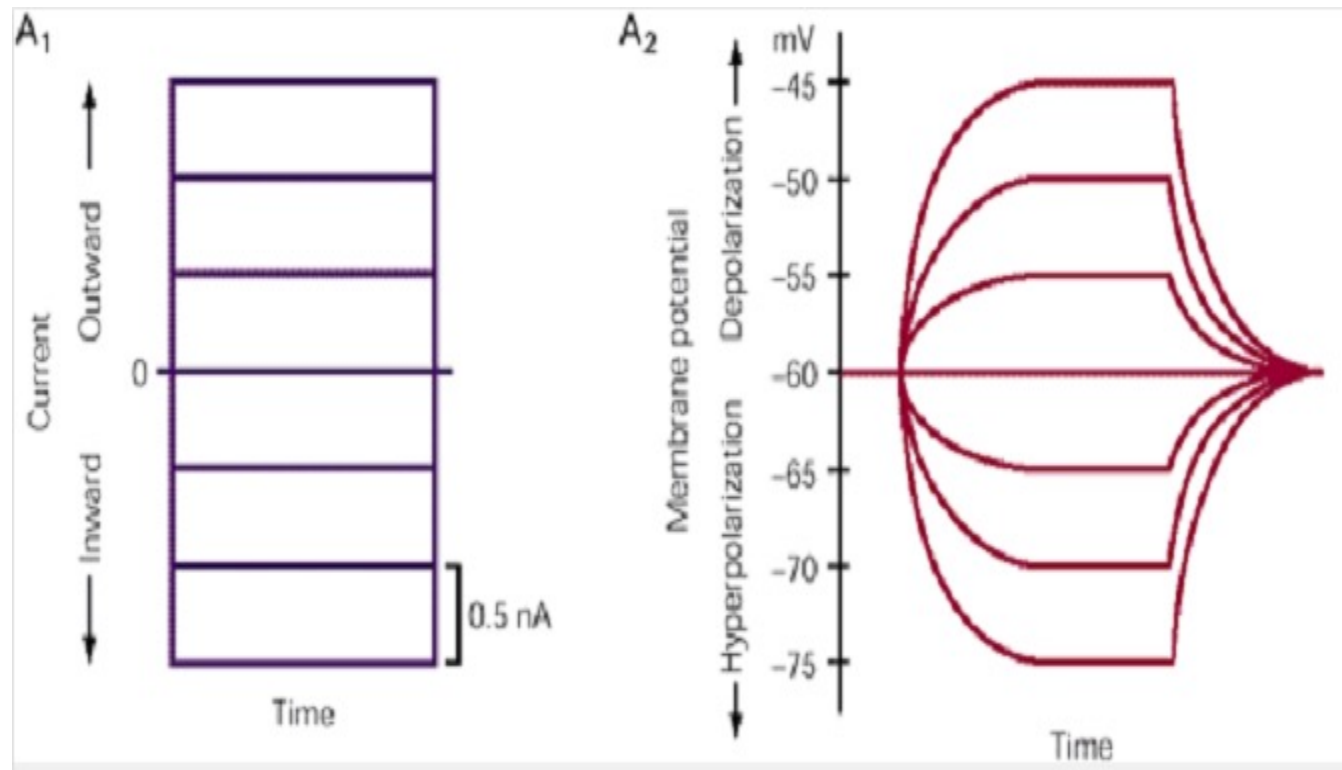
# Current injection across the isopotential cell



# Calculating the membrane resistance

- How can you use a current injection step to experimentally measure the membrane resistance for an isopotential cell?

# Isopotential cell: membrane resistance


- Once  $V_m$  reaches steady state, the governing equation for the entire cell is:

$$V_m - V_{rest} = I_{inj} R_m$$

- where  $R_m$  represents the membrane resistance of the entire cell

# Isopotential cell: membrane resistance

$$R_m = (V_m - V_{rest}) / I_{inj}$$

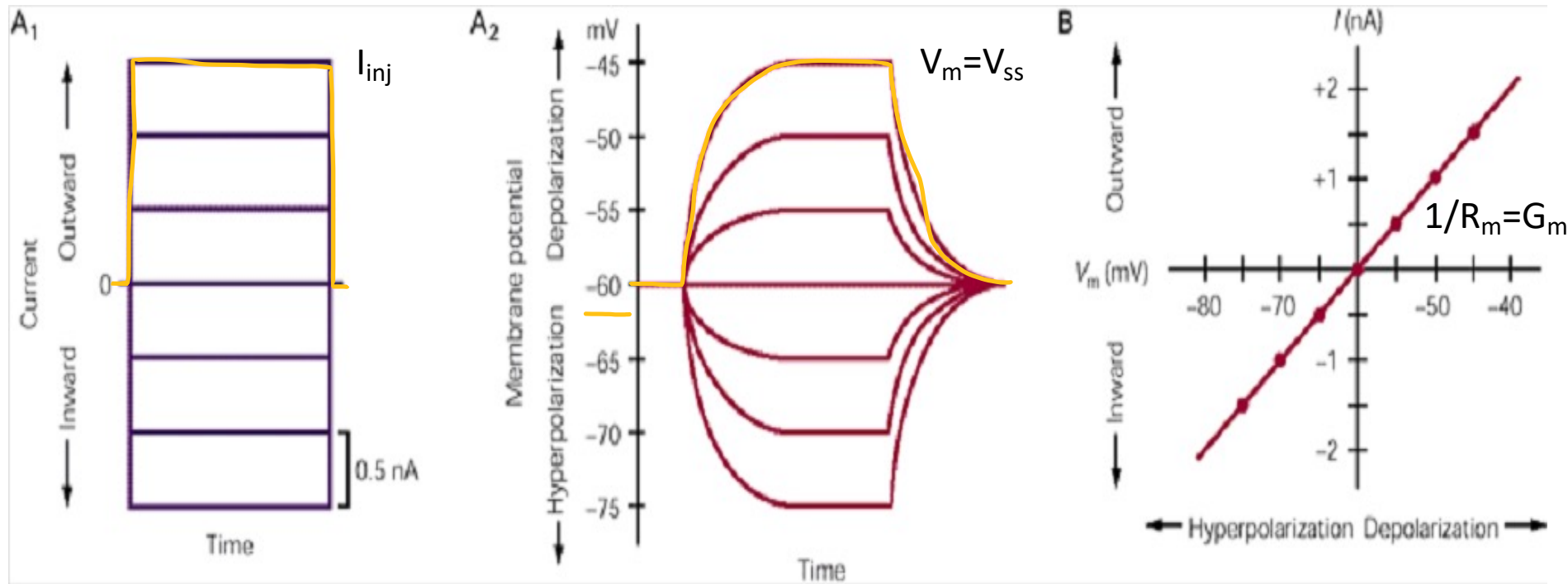

# Calculating the membrane capacitance

- How do you experimentally measure the membrane capacitance for an isopotential cell?

$$V = V_0 \left( 1 - e^{-\frac{t}{RC}} \right)$$

$$\begin{aligned} e &= 2.718 \\ 1/e &= 0.368 \\ 1 - 1/e &= 0.632 \end{aligned}$$



# Isopotential cell : membrane capacitance

- How do you experimentally measure the membrane capacitance for an isopotential cell?

$$V = V_0 \left(1 - e^{-\frac{t}{RC}}\right)$$

- $V_0 = V_{ss} = I_{inj} * R$

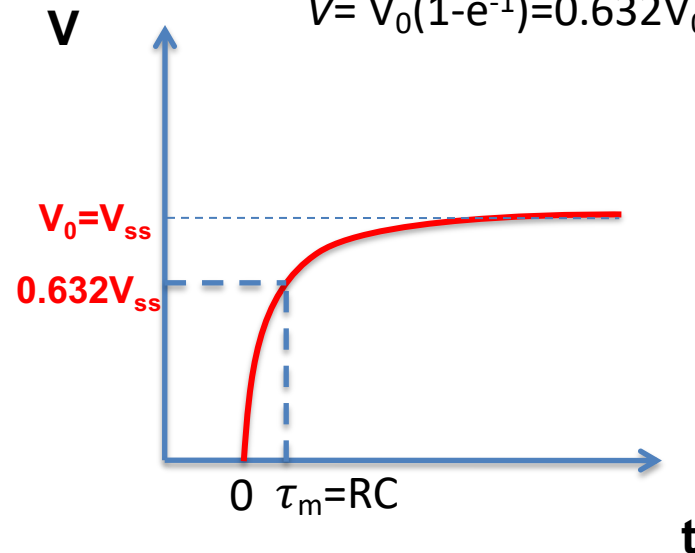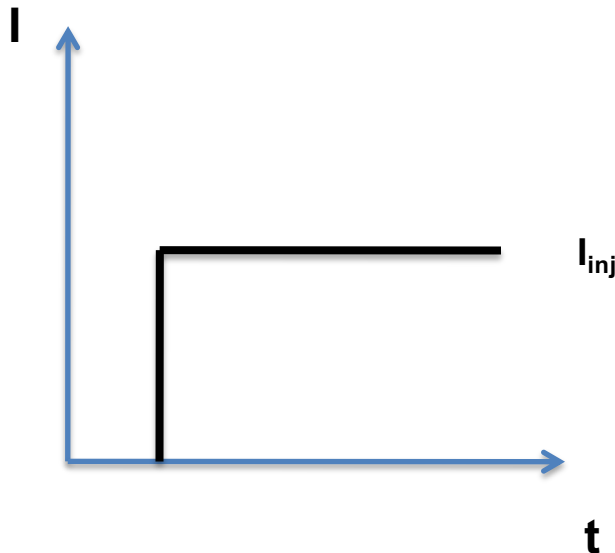- When  $t = RC = \tau_m$   
 $V = V_0(1 - e^{-1}) = 0.632V_0$



$$\begin{aligned} e &= 2.718 \\ 1/e &= 0.368 \\ 1 - 1/e &= 0.632 \end{aligned}$$

How do  $C_m$  and  $R_m$  establish the input (current injection) and output ( $V_m$ ) relationship for the isopotential neuron?

# Specific membrane resistance and capacitance

You can also estimate the membrane resistance and capacitance if you know the cell's

1. Geometry
2. Specific membrane resistance
3. Specific membrane capacitance



# Specific membrane resistance

$R_M$  is the specific membrane resistance( $\Omega \cdot \text{cm}^2$ ).

- This value differs significantly between neural cell types.
- How would you calculate the total resistance for the entire cell membrane ( $R_m$ )?

# Membrane resistance for an isopotential cell

$$R_m = \frac{R_M}{4\pi a^2}$$


- $a$  is the spherical cell's radius
- $R_m$  is proportional to  $R_M$ 
  - $R_m$  is not the same for every neuron  $\rightarrow$  different membrane surface areas or different  $R_M$
- How does the size of the cell affect its  $R_m$ ?

# Membrane resistance for an isopotential cell

$$R_m = \frac{R_M}{4\pi a^2}$$

- $a$  is the spherical cell's radius
- $R_m$  is inversely proportional to the surface area
  - the smaller the radius, the higher the  $R_m$

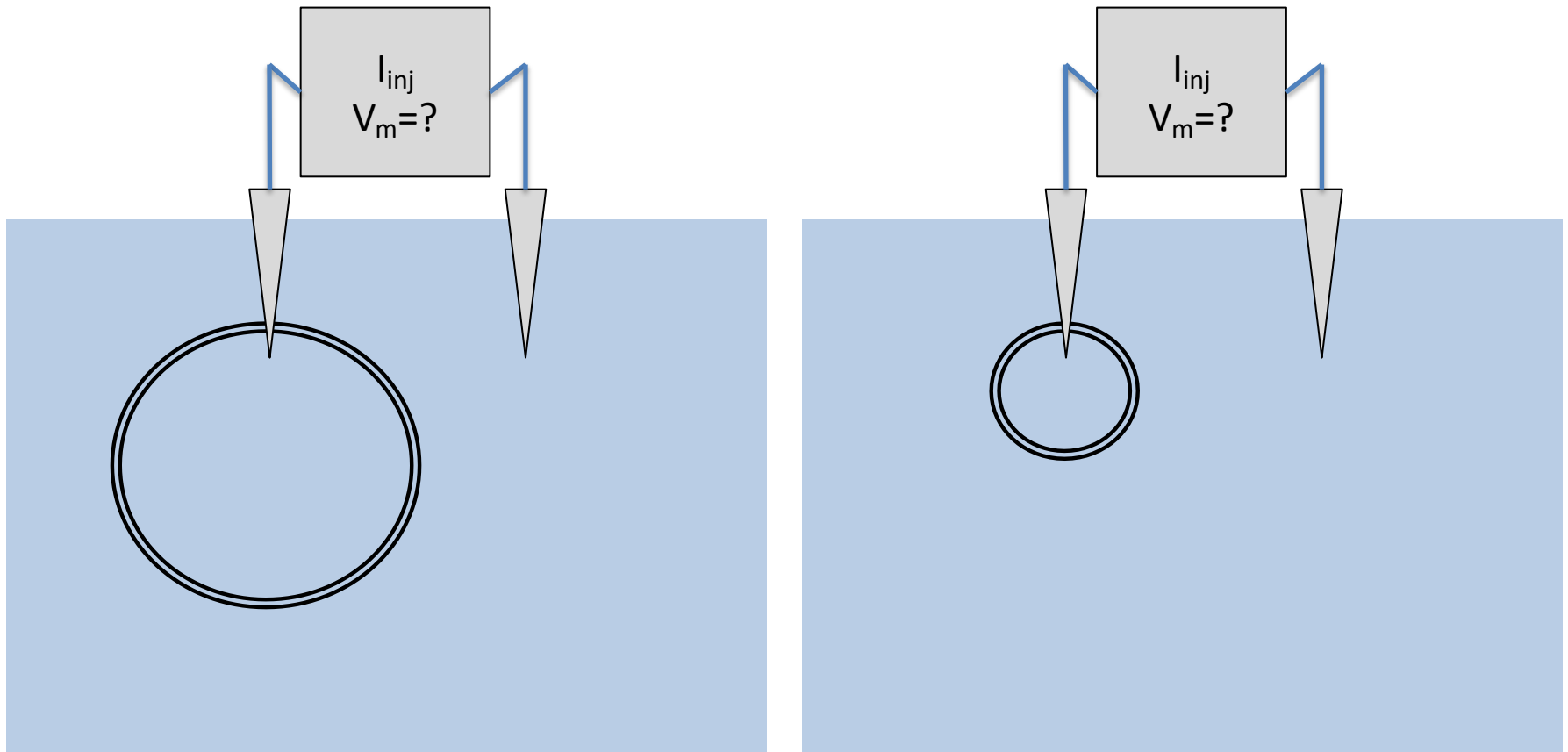Which one has a higher  $V_m$  with  $I_{inj}$ ?



# Specific membrane capacitance


$C_M$  is the specific membrane capacitance ( $\mu\text{F}/\text{cm}^2$ ).

- This value remains highly consistent across neural cell types (approximately  $1\mu\text{F}/\text{cm}^2$ ).
- How would you calculate the capacitance for the entire cell membrane?
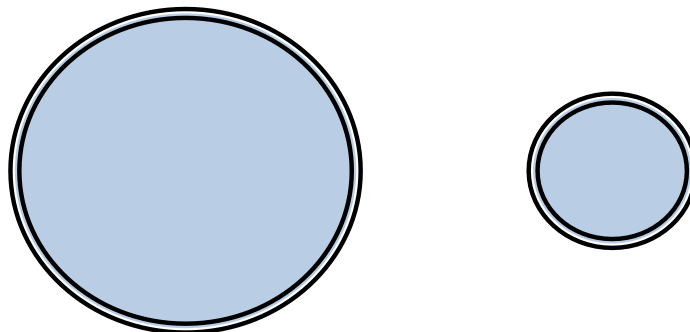
# Specific membrane capacitance

$C_M$  is the specific membrane capacitance ( $\mu\text{F}/\text{cm}^2$ ).

- This value remains highly consistent across neural cell types (approximately  $1\mu\text{F}/\text{cm}^2$ ).
- Which cell has the larger capacitance?



# Limitations for our isopotential cell model, Part 1


- Subthreshold signals traverse the whole cell, not just the soma
  - Dendrites
  - Axons
- The signals decrease in amplitude as a function of distance travelled
- We ignore axial resistance  $R_a$  in our models (because our neuron is a sphere) but will return to it in the next lecture

# Limitations for our isopotential cell model, Part 2


- With our simple RC circuit model of an isopotential cell, we can estimate ***passive*** membrane properties from current clamp experiments.
- However, our model does not accommodate ***active*** membrane properties (ex. Spikes!!). This will be covered in future lectures.



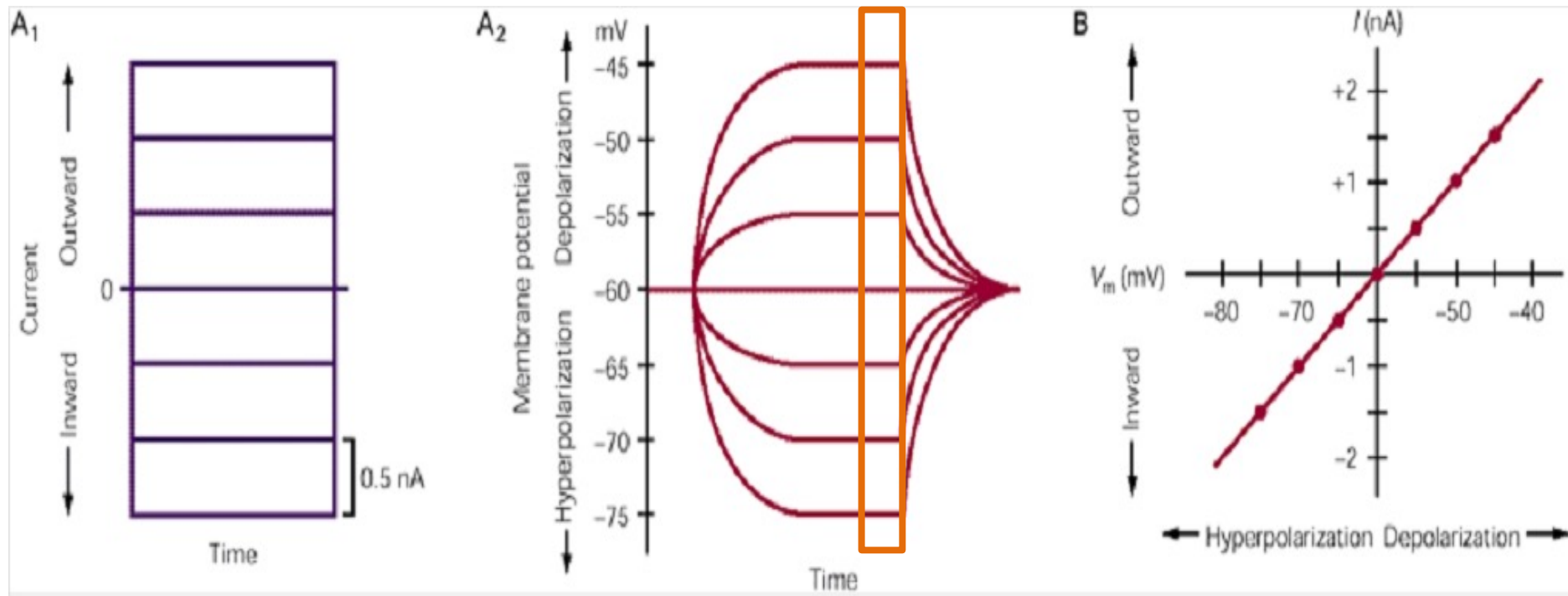
# Current injection across an isopotential cell



# Real current injection experiments

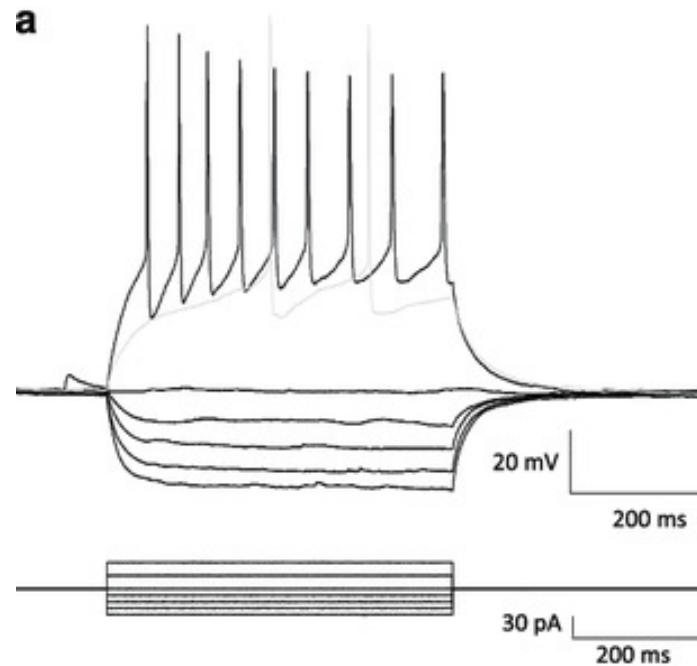

# Real current injection experiments

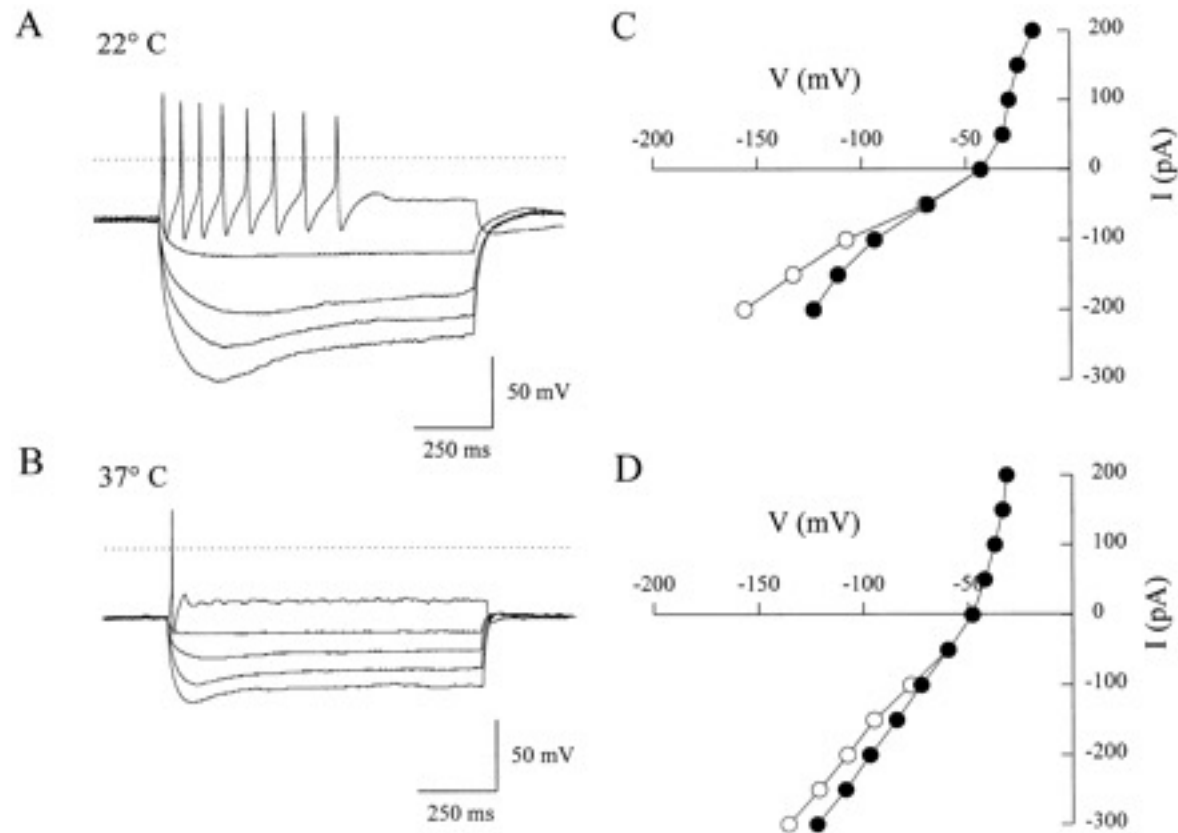

J. Cuevas et al. Journal of Neurophysiology. 1997

# Additional Readings

Paul Miller

Ch 2.2

An Introductory Course in

**COMPUTATIONAL  
NEUROSCIENCE**

Electronics for electrophysiologists

Boris Barbour<sup>\*†</sup>

September 17, 2014

## **Chapter 1**

### **The Hodgkin–Huxley Equations**

G.B. Ermentrout and D.H. Terman, *Mathematical Foundations of Neuroscience*,  
Interdisciplinary Applied Mathematics 35, DOI 10.1007/978-0-387-87708-2\_1,  
© Springer Science+Business Media, LLC 2010

# Reading Ahead

Neuron  
Obituary

**Wilfrid Rall (1922–2018)**

## **Chapter 1**

### **The Hodgkin–Huxley Equations**

G.B. Ermentrout and D.H. Terman, *Mathematical Foundations of Neuroscience*,  
Interdisciplinary Applied Mathematics 35, DOI 10.1007/978-0-387-87708-2\_1,  
© Springer Science+Business Media, LLC 2010

# Next time

- Introduction to cable theory (Video on Bb Learn will be available Tuesday)

Lab 1 is due Monday at 11:59 PM